

Tutorial - 3

Problem ① :

$$V_{\text{ref}} = \sin(2\pi 50t)$$

$$\therefore \bar{V} = V \angle 0^\circ$$

$$\therefore \bar{V}_s(t) = V \sin(2\pi 50t)$$

$$\bar{I} = I \angle -\theta$$

$$i(t) = I \sin(2\pi 50t - \theta)$$

$$R\bar{I} = \bar{V}_R = RI \angle -\theta$$

$$V_R(t) = RI \sin(2\pi 50t - \theta)$$

$$\bar{V}_L = j\omega L \bar{I} = \omega LI \angle 90^\circ - \theta$$

$$V_L(t) = \omega LI \sin(2\pi 50t + 90^\circ - \theta)$$

New reference : $\sin(2\pi 50(t-0.005)) = \sin(2\pi 50t - \pi/2)$


With new reference,

$$\bar{V} = V \angle \pi/2$$

$$\bar{I} = I \angle \pi/2 - \theta$$

$$R\bar{I} = RI \angle \pi/2 - \theta$$
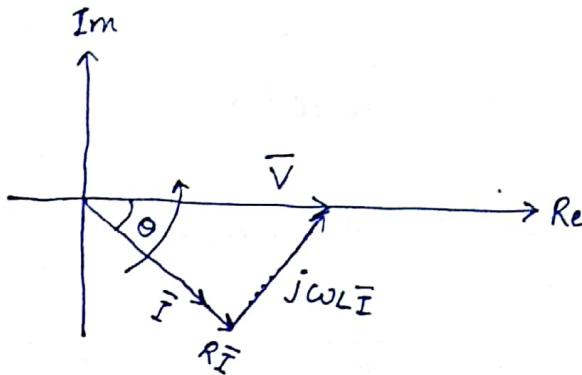
$$\bar{V}_L = \omega LI \angle \pi - \theta$$



Problem ② :


i) $V(t) = 100 \sin(2\pi 50t)$ volts = $100 \angle 0^\circ$ volts

$$\omega = 2\pi \times 50 \text{ rad/s}$$

$$Z_L = j\omega L = j(2\pi 50)(0.05) = j15.71 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(2\pi \times 50)(100 \times 10^{-6})} = -j31.83 \Omega$$
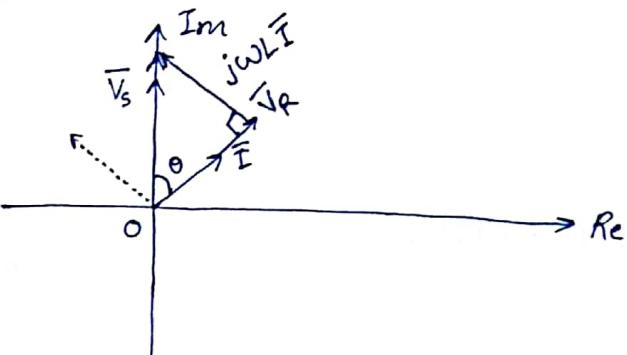
$$\therefore Z = R + Z_L + Z_C = 10 + j15.71 - j31.83 = 10 - j16.12$$



$$Z = 10 - j16 \cdot 12 = 18.96 \angle -58.18^\circ \Omega$$

$$\therefore I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{18.96 \angle -58.18^\circ} = 5.274 \angle 58.18^\circ$$

$$\therefore I(t) = 5.274 \sin(2\pi 50t + 58.18^\circ) \text{ Amps}$$

(ii) $I = \frac{V \angle \theta}{R + j(\omega L - \frac{1}{\omega C})} = \frac{V}{Z}$

$$|I| = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

For maximum current, i.e., for maximum $|I|$

$$\frac{d|I|}{dc} = 0 \Rightarrow \text{solving this, we get, } \omega L - \frac{1}{\omega C} = 0$$

$$\therefore C = \frac{1}{\omega^2 L}$$

Alternatively, $|I| = \frac{|V|}{|Z|}$. Now, $|I|$ will be maximum when $|Z|$ is minimum.

$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

We can see that $|Z|$ will be minimum only when $\omega L - \frac{1}{\omega C} = 0$

$$\text{i.e. } \omega L = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega^2 L}$$

$$C = \frac{1}{(2\pi 50)^2 (0.05)} = 202.64 \mu F$$

Under this condition, $Z = 10 + j0 = 10$

$$\therefore I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{10}$$

$$\therefore I = 10 \angle 0^\circ$$

$$I(t) = 10 \sin(2\pi 50t) \text{ Amps.}$$

$$V_L(t) = \chi_L I(t) = (j\omega L)(10 \sin(2\pi 50t))$$

$$= j(2\pi \times 50)(0.05)(10) \sin(2\pi 50t)$$

$$= (j157.08) \sin(2\pi 50t)$$

$$V_L(t) = 157.08 \sin(2\pi 50t + 90^\circ) \text{ volts.}$$


Similarly, $V_C(t) = \chi_c I(t) = \frac{-j}{(2\pi 50)(202.64 \times 10^{-6})} \times 10 \sin(2\pi 50t)$

$$= (-j157.08) \sin(2\pi 50t)$$

$$V_C(t) = 157.08 \sin(2\pi 50t - 90^\circ) \text{ volts.}$$

Amplitudes of $V_L(t)$ and $V_C(t)$ are equal (i.e., 157.08 volts), and, amplitudes of $V_L(t)$ and $V_C(t)$ are higher than amplitude of $V_S(t)$ (i.e., 100 v).

Problem ③ :

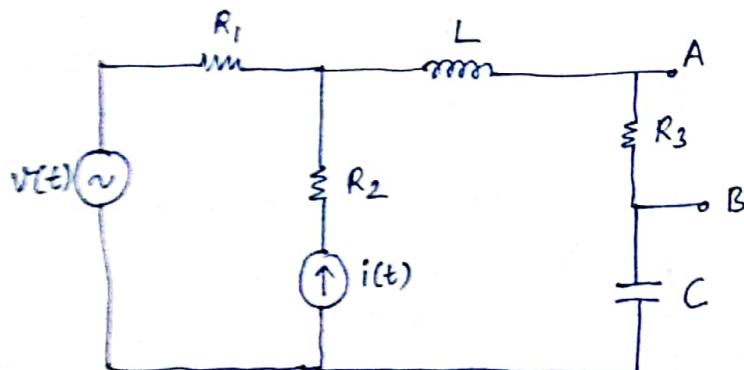

$$V(t) = 50 \sin(2\pi 50t + 30^\circ) \text{ v} = 50 \angle 30^\circ \text{ v}$$

$$i(t) = 10 \sin(2\pi 50t - 10^\circ) \text{ A} = 10 \angle -10^\circ \text{ A}$$


$$R_1 = 5\Omega, R_2 = 3\Omega, L = 10mH, R_3 = 2\Omega, C = 0.8mF$$

To find: $V_R(t)$ expression across R_3

Converting to phasor-form,


$$X_L = j\omega L = j(2\pi \times 50)(10^{-2}) = -\pi/90^\circ \Omega$$
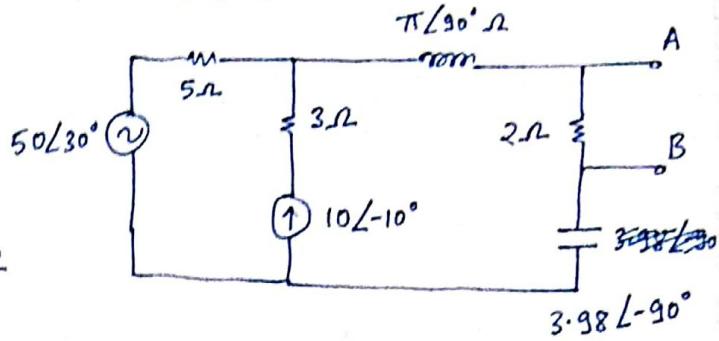
$$X_C = \frac{-j}{\omega C} = \frac{-j}{(2\pi \times 50)(0.8 \times 10^{-3})} = 3.98/-90^\circ \Omega$$




Applying Thévenin's equivalent across A-B :

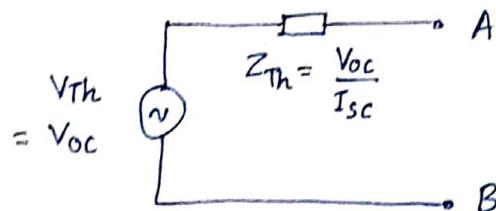NOTE : For Thévenin's theorem, first we calculate V_{OC} (open circuit voltage) followed by calculation of I_{SC} (short circuit current) and then drawing the equivalent circuit across A and B like :




But as given circuit contains no dependent sources, we can compute Z_{Th} by replacing all independent sources with their equivalent impedances and finding total impedance across A-B .

(a) Calculating V_{OC} :

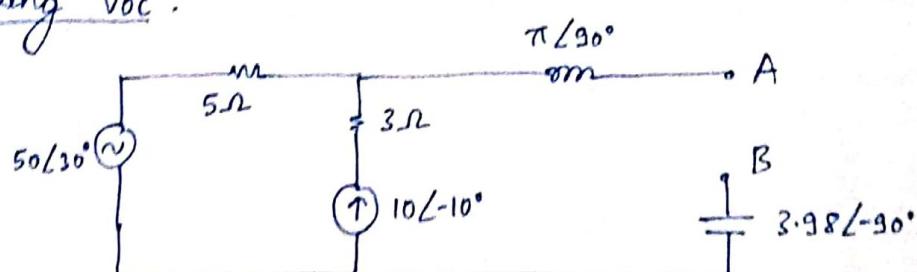


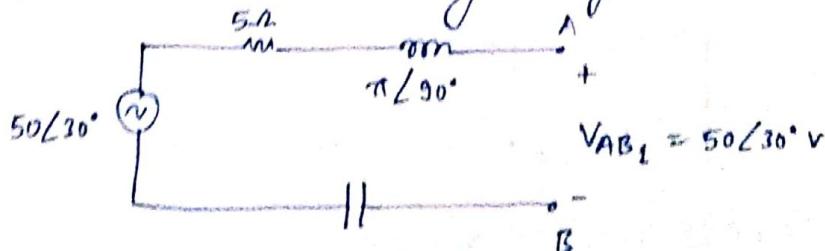Apply Superposition : Considering voltage source :



$$V_{AB1} = 50\angle 30^\circ V$$

Considering current source:

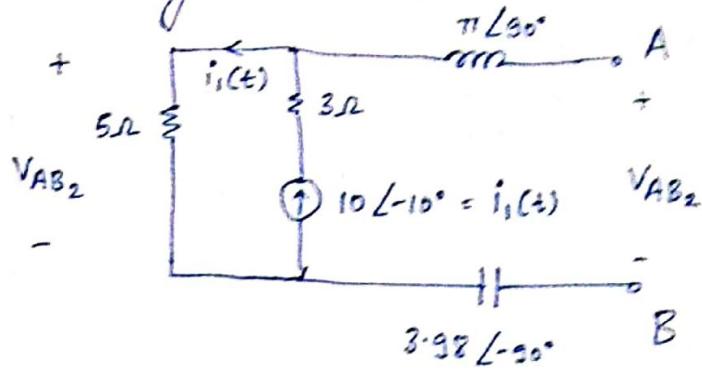


All current will pass through
5Ω branch as open circuit will
not allow current to pass.


$$\text{so, } V_{AB_2} = \text{Voltage drop across } 5\Omega = 5 \times 10 \angle -10^\circ \\ = 50 \angle -10^\circ \text{ V.}$$

$$\text{so total } V_{AB} = V_{AB_1} + V_{AB_2} = 50 \angle 30^\circ + 50 \angle -10^\circ = 93.97 \angle 10^\circ \quad \text{--- (1)}$$

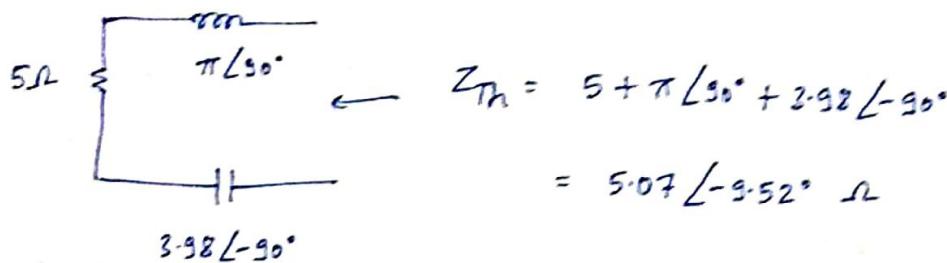Calculating Z_{Th} : Replace all sources with their equivalent impedances and calculate Z_{AB} .



Thermin's equivalent:


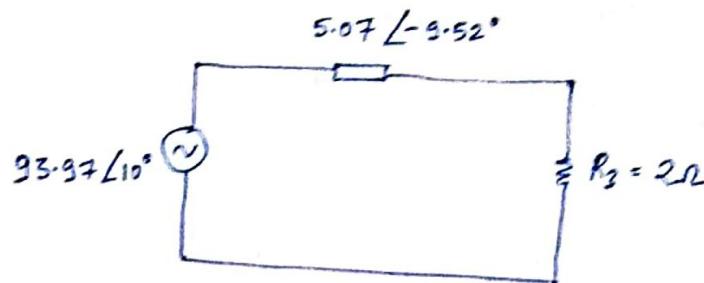


$$\text{so } V_R(t) = \frac{R_3 \times V_{oc}}{R_3 + Z_{Th}} = \frac{2}{(2 + 5.07 \angle -9.52^\circ)} \times (93.97 \angle 10^\circ)$$

$$V_R(t) = 26.65 \angle 16.83^\circ$$

$$\hat{V}_R(t) = 26.65 \sin(2\pi 50t + 16.83^\circ)$$

Problem 4 :

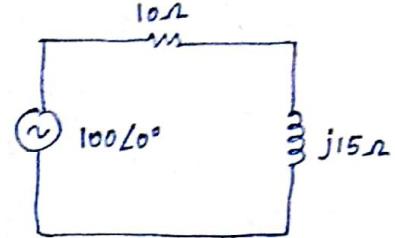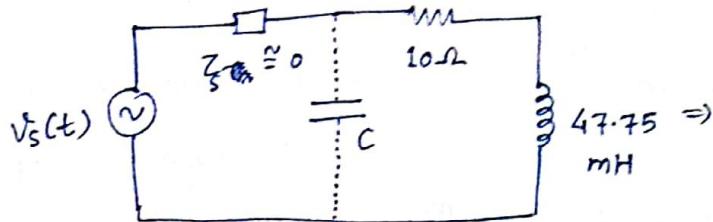

$$V_s(t) = 100 \sin(2\pi 50t) = 100\angle 0^\circ$$

$$\therefore f = 50 \text{ Hz} \Rightarrow \omega = 2\pi \times 50 \text{ rad/sec}$$

$$X_L = 2\pi f L = 2\pi \times 50 \times 47.75 \times 10^{-3} = 15\Omega$$

$$\text{Now, } \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{100\angle 0^\circ}{R + jX_L} = \frac{100\angle 0^\circ}{10 + j15} = \frac{100\angle 0^\circ}{18.03 \angle 56.31^\circ}$$

$$\bar{I} = 5.546 \angle -56.31^\circ \text{ Amps.}$$

Phase difference between \bar{V} & \bar{I} : $\phi = 56.31^\circ$.

$$\therefore \text{PF} = \cos \phi = \cos(56.31^\circ) = 0.5547 \text{ (lag)} \quad \left[\text{or } \cos \phi = \frac{R}{\sqrt{R^2 + X_L^2}} \right]$$

$$\begin{aligned} P &= \text{Real} \left(\bar{V}_{\text{rms}} \cdot \bar{I}_{\text{rms}}^* \right) \\ &= \text{Real} \left(\frac{\bar{V}}{\sqrt{2}} \cdot \frac{\bar{I}}{\sqrt{2}}^* \right) \\ &= \frac{1}{2} \text{ Real part of} \left(\bar{V} \bar{I}^* \right) \\ &= \frac{1}{2} \text{ Real} \left((100\angle 0^\circ) (5.546 \angle +56.31^\circ) \right) \\ &= \frac{1}{2} \text{ Real} \left[554.6 \angle 56.31^\circ \right] \end{aligned}$$

$$P = 153.85 \text{ Watts.}$$

$$Q = \text{Imaginary} \left(\bar{V}_{\text{rms}} \bar{I}_{\text{rms}}^* \right) = \text{Imag} \left(\frac{\bar{V}}{\sqrt{2}} \cdot \frac{\bar{I}}{\sqrt{2}}^* \right) = \frac{1}{2} \text{ Imag} \left(\bar{V} \cdot \bar{I}^* \right)$$

$$Q = \frac{1}{2} \operatorname{Imag} \left[(100 \angle 0^\circ) \cdot (5.546 \angle +56.31^\circ) \right]$$

$Q = 230.77 \text{ VAR} \longrightarrow (\text{This is 'Q' supplied by } V_s)$

New power factor = 0.95 lag

(after adding 'C')

$$\cos \phi_n = \frac{P}{\sqrt{P^2 + Q_n^2}} \Rightarrow Q_n = \left[\left(\frac{P}{\cos \phi_n} \right)^2 - P^2 \right]^{1/2}$$

$$Q_n = \left[\left(\frac{153.85}{0.95} \right)^2 - (153.85)^2 \right]^{1/2} = 50.568 \text{ VAR}$$

' Q_n ' is the new Q supplied by V_s . So the difference of previous Q supplied by V_s and new Q supplied by V_s has to come from capacitor.

$$\therefore Q_C = 230.77 - 50.568 = 180.2 \text{ VAR}$$

$$\text{Now, } \bar{I}_c = \frac{\bar{V}_c}{\left(\frac{-j}{\omega C}\right)} = (j\omega C)\bar{V} \quad (\bar{V}_c = \bar{V}, \text{ see from figure})$$

$$\therefore Q_C = \text{Imaginary part of } \left\{ \bar{V}_{\text{rms}} \bar{I}_{C_{\text{rms}}}^* \right\}$$



$$= \operatorname{Imag} \left\{ \frac{\bar{V}}{\sqrt{2}} \cdot \frac{\bar{I}_c^*}{\sqrt{2}} \right\} = \frac{1}{2} \operatorname{Imag} \left[\bar{V} \bar{I}_c^* \right]$$

$$= \frac{1}{2} \operatorname{Imag} \left[\bar{V} (-j\omega C \bar{V}) \right]$$

$$Q_C = \frac{1}{2} \omega C V^2 \Rightarrow C = \frac{2Q_C}{\omega V^2} = \frac{2 \times 180.2}{(2\pi \times 50) \times (100)^2}$$

$$C = 114.72 \mu\text{F}$$

Problem 5 :

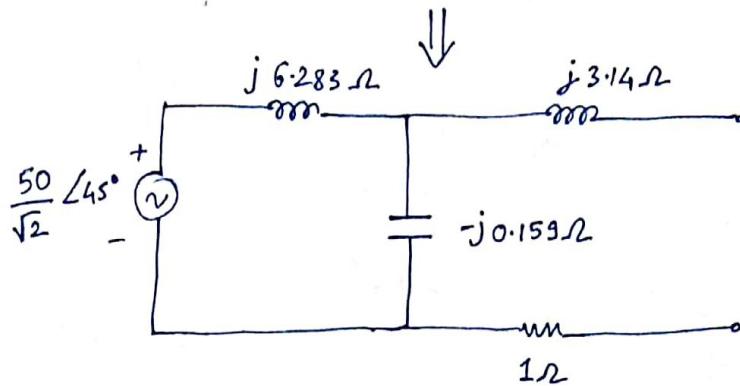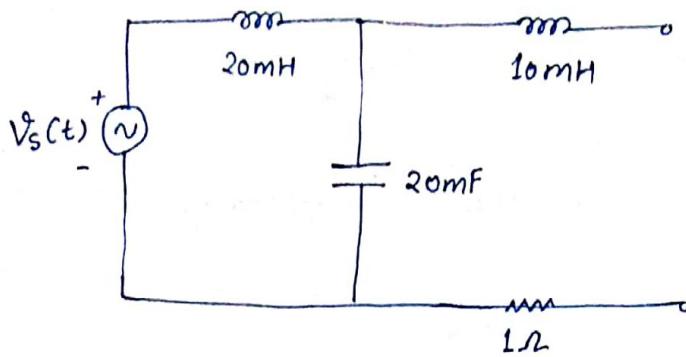

$$\text{Here, } V_s(t) = 50 \sin(2\pi 50t + 45^\circ) \text{ volts}$$


$$\bar{V}_s = \frac{50}{\sqrt{2}} \angle 45^\circ \text{ volts} = \frac{50}{\sqrt{2}} \angle 45^\circ \text{ volts}$$

$$\bar{Z}_{th} = j3.14 + (j6.283 \parallel -j0.159) + 1 = 1 + j2.977 \Omega$$

and $\bar{V}_{th} = \frac{\bar{V}_s \times (-j0.159)}{j6.283 - j0.159} = \bar{V}_s \times (-0.0259)$

$$\bar{V}_{th} = \frac{50}{\sqrt{2}} \times 0.0259 \angle 45^\circ + 180^\circ$$
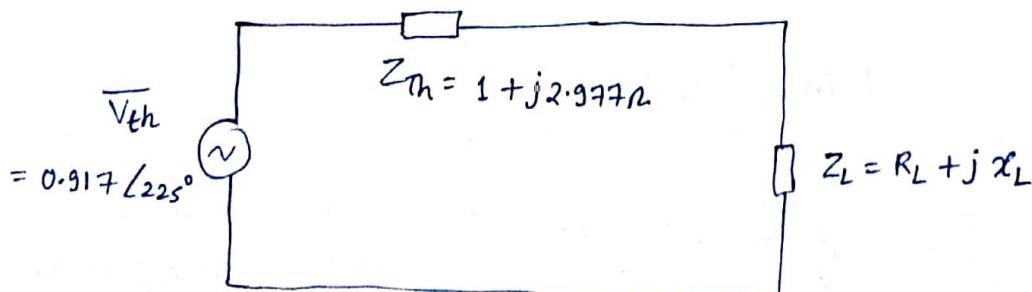
$$\bar{V}_{th} = 0.917 \angle 225^\circ$$



Now, $P_L = \text{Real part of } (\bar{V}_L \cdot \bar{I}^*)$

$$\bar{V}_L = \frac{\bar{V}_{th} \cdot Z_L}{Z_L + Z_{th}} = \frac{\bar{V}_{th} (R_L + jX_L)}{R_L + jX_L + 1 + j2.977}$$

$$\bar{V}_L = \frac{\bar{V}_{th} \cdot (R_L + jX_L)}{(1 + R_L) + j(X_L + 2.977)}$$

$$\bar{I} = \frac{\bar{V}_{th}}{R_L + jX_L + 1 + j2.977} = \frac{\bar{V}_{th}}{(R_L + 1) + j(X_L + 2.977)}$$

$$\bar{I}^* = \frac{\bar{V}_{th}^*}{(R_L + 1) - j(X_L + 2.977)}$$

$$\therefore P_L = \text{Real part of } \left[\bar{V}_L \cdot \bar{I}^* \right] = \text{Real} \left\{ \left(\frac{\bar{V}_{th} (R_L + jX_L)}{(R_L + 1) + j(X_L + 2.977)} \right) \left(\frac{\bar{V}_{th}^*}{(R_L + 1) - j(X_L + 2.977)} \right) \right\}$$

$$P_L = \text{Real part} \left\{ \frac{|V_{th}|^2 (R_L + jX_L)}{(R_L + 1)^2 + (X_L + 2.977)^2} \right\}$$

$$P_L = \frac{|V_{th}|^2 R_L}{(R_L + 1)^2 + (X_L + 2.977)^2}$$

$$\text{Now, } \frac{\partial P_L}{\partial Z_L} = \frac{\partial P_L}{\partial R_L} \cdot \frac{\partial R_L}{\partial Z_L} + \frac{\partial P_L}{\partial X_L} \cdot \frac{\partial X_L}{\partial Z_L}$$

$$\text{Now, for max. power, } \frac{\partial P_L}{\partial Z_L} = 0$$

$$Z_L^2 = R_L^2 + X_L^2 \Rightarrow \frac{\partial Z_L}{\partial R_L} = \frac{R_L}{Z_L} \Rightarrow \frac{\partial R_L}{\partial Z_L} = \frac{Z_L}{R_L}$$

$$\therefore \frac{\partial R_L}{\partial Z_L} = \frac{\sqrt{R_L^2 + X_L^2}}{R_L}$$

$$\text{Similarly, } \frac{\partial Z_L}{\partial x_L} = \frac{x_L}{Z_L} \Rightarrow \frac{\partial x_L}{\partial Z_L} = \frac{Z_L}{x_L} = \frac{\sqrt{R_L^2 + x_L^2}}{x_L}$$

$$\text{For } \frac{\partial P_L}{\partial Z_L} = 0 \Rightarrow \frac{\partial P_L}{\partial x_L} = 0 \text{ and } \frac{\partial P_L}{\partial R_L} = 0$$

$$\frac{\partial P_L}{\partial x_L} = \frac{-2|V_{th}|^2 R_L (x_L + x_{th})}{[(R_L + R_{th})^2 + (x_L + x_{th})^2]^2} = 0$$

This gives us $\underline{x_L = -x_{th}}$


$$\begin{aligned} \text{Similarly, } \frac{\partial P_L}{\partial R_L} &= \cancel{\frac{[(R_L + R_{th})^2 + (x_L + x_{th})^2] \cdot |V_{th}|^2 - (2R_L(R_L + R_{th}))|V_{th}|^2}{[(R_L + R_{th})^2 + (x_L + x_{th})^2]^2}} \\ &= \frac{(|V_{th}|^2) \cdot [(x_{th} + x_L)^2 + (R_{th} - R_L)(R_{th} + R_L)]}{[(R_L + R_{th})^2 + (x_L + x_{th})^2]^2} \\ \frac{\partial P_L}{\partial R_L} = 0 &\Rightarrow \underline{R_{th} = R_L} \quad (\underline{x_{th} + x_L \text{ also } = 0 \text{ from previous part}}) \end{aligned}$$

$$\therefore Z_L = R_L + jx_L = R_{th} - jx_{th}$$

$$\therefore \underline{Z_L = Z_{th}^*}$$

$$\therefore Z_L = 1 - j2.977 \Omega$$


Problem ⑥ :

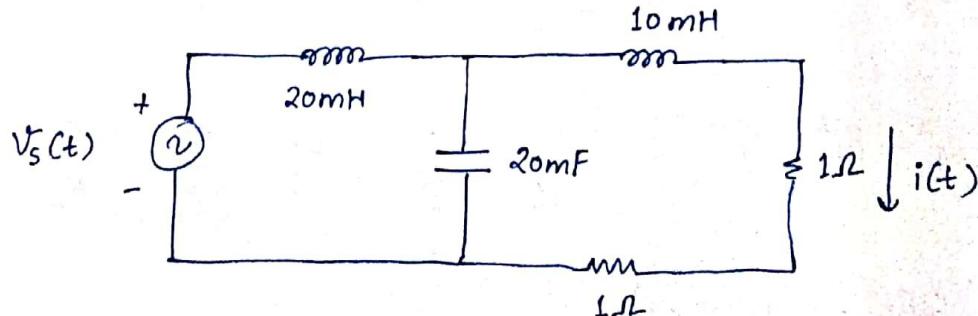

$$V_S(t) = 50 \sin(100t - 25^\circ) \text{ V}$$

Here, $\omega = 100 \text{ rad/s}$. Reference phasor: $\sin(100t)$

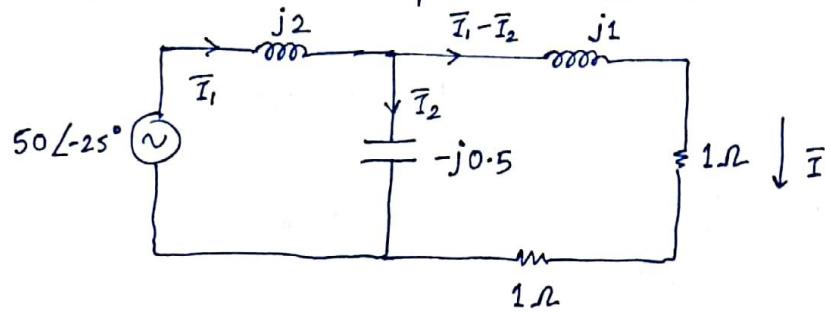∴ The equivalent circuit in phasor domain is :



Applying KVL, we get,

$$50\angle -25^\circ = \bar{I}_1(j_2) + \bar{I}_2(-j0.5) \quad \dots \textcircled{1}$$

$$\bar{I}_2(-j0.5) - (\bar{I}_1 - \bar{I}_2)(j_1) - 2(\bar{I}_1 - \bar{I}_2) = 0$$

$$\text{or, } (2+j_1)\bar{I}_1 = (2+j0.5)\bar{I}_2$$

$$\bar{I}_1 = \frac{(2+j0.5)}{2+j_1} \bar{I}_2 \quad \dots \textcircled{2}$$

Substitute \textcircled{2} in \textcircled{1},

$$50\angle -25^\circ = \left(\frac{-1+j4}{2+j_1} - j0.5 \right) \bar{I}_2$$


$$= \frac{(-1+j4 - j1 + 0.5)}{2+j_1} \bar{I}_2 = \left(\frac{-0.5+j3}{2+j_1} \right) \bar{I}_2$$

$$(50\angle -25^\circ) = (1.35\angle 72.89^\circ) \bar{I}_2 \Rightarrow \bar{I}_2 = 37.03\angle -97.89^\circ \text{ Amp.}$$

$$\bar{I}_1 = \left(\frac{2+j0.5}{2+j_1} \right) \bar{I}_2$$

$$\bar{I} = \bar{I}_1 - \bar{I}_2 = 8.21\angle 145.53^\circ \text{ Amp.}$$

Thevenin's theorem :

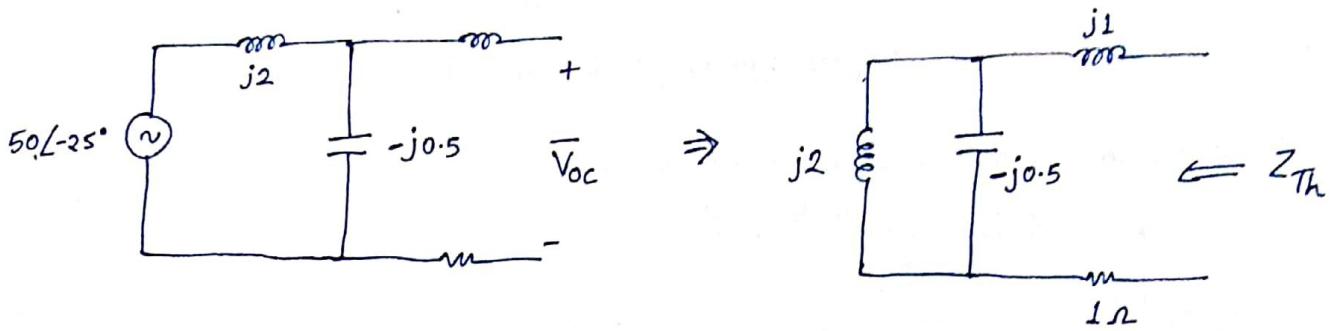


$$\overline{V_{oc}} = (50 \angle -25^\circ) \times \frac{-j0.5}{j2 - j0.5} = -16.66 \angle -25^\circ \text{ Volts}$$

$$\overline{V_{oc}} = 16.66 \angle 155^\circ \text{ Volts}$$

$$\overline{Z_{Th}} = (j2 || -j0.5) + j1 + 1 = \frac{j2 \times (-j0.5)}{j2 - j0.5} + 1 + j1$$

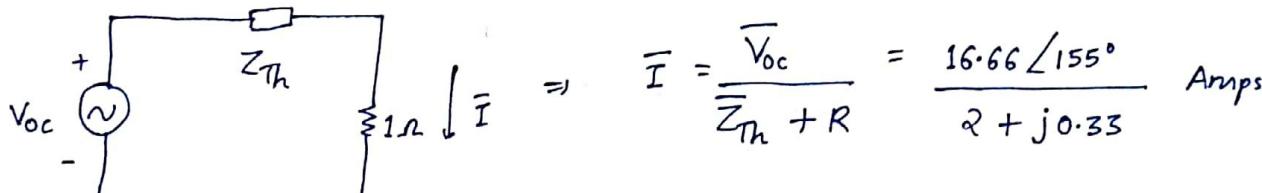
$$\overline{Z_{Th}} = -j0.66 + 1 + j1 = 1 + j0.33$$



$$\overline{I} = \frac{\overline{V_{oc}}}{\overline{Z_{Th}} + R} = \frac{16.66 \angle 155^\circ}{2 + j0.33} = 8.20 \angle 145.63^\circ \text{ Amps}$$

$$\therefore i(t) = 8.20 \sin(100t + 145.63^\circ) \text{ Amps.}$$

Problem ⑦ :

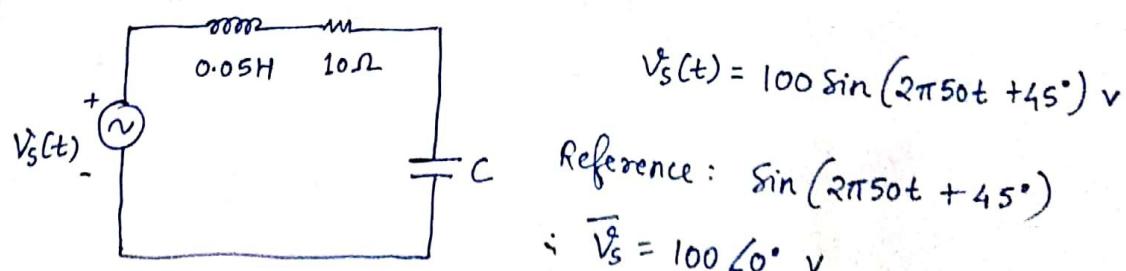

$$\text{Reference: } \sin(2\pi 50t + 45^\circ)$$

$$\therefore \overline{V_s} = 100 \angle 0^\circ \text{ v}$$

$$\overline{Z} = R + j\omega L - j\left(\frac{1}{\omega C}\right) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\text{For } C = 150\mu\text{F}, \quad \bar{Z} = 10 + j\left(2\pi \times 50 \times 0.05 - \frac{1}{2\pi \times 50 \times 150 \times 10^6}\right)$$

$$\bar{Z} = 10 + j(15.7 - 21.22) = 10 - j5.51 \Omega = 11.42 \angle -28.85^\circ \Omega$$

$$\bar{I} = \frac{\bar{V}_s}{\bar{Z}} = \frac{100 \angle 0^\circ}{11.42 \angle -28.85^\circ} = 8.756 \angle 28.85^\circ \text{ Amp}$$

$$\bar{V}_R = \bar{I} \cdot R = (10)(8.756) \angle 28.85^\circ = 87.56 \angle 28.85^\circ \text{ volt.}$$

$$\bar{V}_L = \bar{I} \cdot j\omega L = (j15.7) \times 8.756 \angle 28.85^\circ = 137.56 \angle 118.85^\circ \text{ volt.}$$

$$\bar{V}_C = \bar{I} \cdot \left(\frac{1}{j\omega C}\right) = \frac{8.756 \angle 28.85^\circ}{(j0.047123)} = 185.81 \angle -61.15^\circ \text{ volt.}$$

$$i(t) = 8.756 \sin(2\pi 50t + 28.85^\circ) \text{ A}$$

$$v_R(t) = 87.56 \sin(2\pi 50t + 28.85^\circ) \text{ v}$$

$$v_L(t) = 137.56 \sin(2\pi 50t + 118.85^\circ) \text{ v}$$

$$v_C(t) = 185.81 \sin(2\pi 50t - 61.15^\circ) \text{ v}$$

For $C = 202.85\mu\text{F}$,

$$\bar{Z} = 10 + j\left(\omega L - \frac{1}{\omega C}\right) = 10 + j\left(2\pi \times 50 \times 0.05 - \frac{1}{2\pi \times 50 \times 202.85 \times 10^6}\right)$$


$$\bar{Z} = 10 + j(15.7 - 15.7) = 10$$

$$\therefore \bar{I} = \frac{\bar{V}_s}{\bar{Z}} = \frac{100 \angle 0^\circ}{10} = 10 \angle 0^\circ \text{ Amp.}$$

$$\bar{V}_R = \bar{I} \cdot R = 100 \angle 0^\circ$$

$$\bar{V}_L = \bar{I} \cdot (j\omega L) = (10 \angle 0^\circ) \cdot (j15.7) = 157 \angle 90^\circ \text{ volt}$$
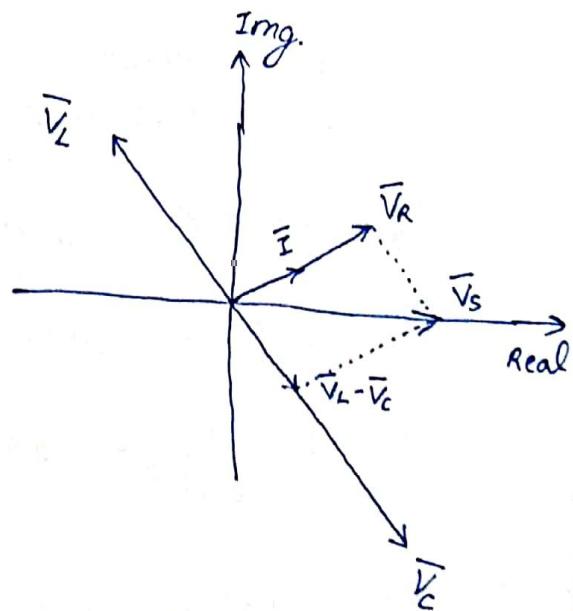
$$\bar{V}_C = \bar{I} \left(\frac{1}{j\omega C}\right) = (10 \angle 0^\circ) (-j15.7) = 157 \angle -90^\circ \text{ volt.}$$




$$i(t) = 10 \sin(2\pi 50t + 45^\circ) A$$

$$V_R(t) = 100 \sin(2\pi 50t + 45^\circ) V$$

$$V_L(t) = 157 \sin(2\pi 50t + 135^\circ) V$$
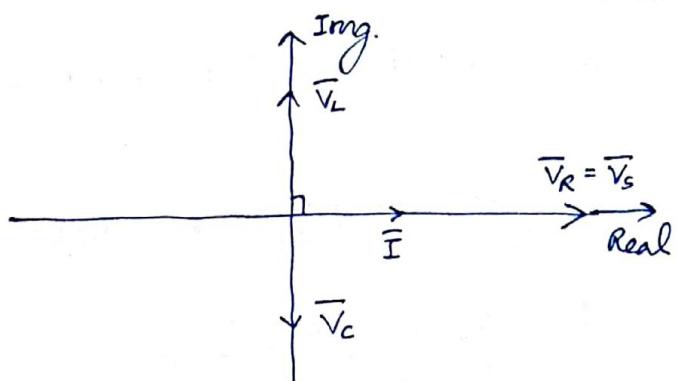
$$V_C(t) = 157 \sin(2\pi 50t - 45^\circ) V$$



For $C = 250 \mu F$,

$$\bar{Z} = 10 + j \left(2\pi \times 50 \times 0.05 - \frac{1}{(2\pi \times 50 \times 250 \times 10^6)} \right) = 10 + j(15.7 - 12.73)$$

$$\bar{Z} = 10 + j2.97 \Omega = 10.43 \angle 16.59^\circ \Omega$$

$$\bar{I} = \frac{\bar{V}_S}{\bar{Z}} = \frac{100 \angle 0^\circ}{10.43 \angle 16.59^\circ} = 9.58 \angle -16.59^\circ$$

$$\bar{V}_R = \bar{I}R = (9.58 \angle -16.59^\circ) \times 10 = 95.8 \angle -16.59^\circ V$$

$$\bar{V}_L = \bar{I}(j\omega L) = (9.58 \angle -16.59^\circ)(j15.7) = 150.623 \angle 73.41^\circ V$$


$$\bar{V}_C = \bar{I} \cdot \left(\frac{1}{j\omega C} \right) = (9.58 \angle -16.59^\circ) \cdot \left(\frac{1}{j2\pi \times 50 \times 250 \times 10^{-6}} \right) = 122.05 \angle -106.59^\circ V$$

$$i(t) = 9.58 \sin(2\pi 50t + 28.41^\circ) A$$

$$V_R(t) = 95.8 \sin(2\pi 50t + 28.41^\circ) V$$

$$V_L(t) = 150.623 \sin(2\pi 50t + 118.41^\circ) V$$
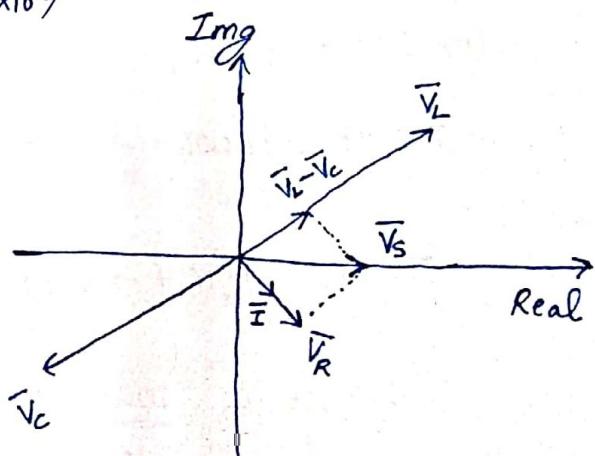
$$V_C(t) = 122.05 \sin(2\pi 50t - 61.59^\circ) V$$



Problem ⑧: $V_s(t) = 100 \sin(2\pi \times 50t + \alpha) \text{ V}$

(i) Switch is closed at $t=0$,

$V_s(t) = 100 \sin(2\pi \times 50t + \alpha)$ can be written as,

$$\bar{V}_s = 100 \angle \alpha$$

$i(t) = \text{Transient response} + \text{Steady state response}$

$$= A e^{-Rt/L} + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t + \alpha - \tan^{-1}(\frac{\omega L}{R}))$$

Inductor doesn't allow sudden change in current, so $i_L(0^-) = i_L(0^+) = 0$

At $t=0$, $i(0) = 0$.

Substituting in above equation,

$$i(0) = A + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\alpha - \tan^{-1}(\frac{\omega L}{R}))$$

$$0 = A + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\alpha - \tan^{-1}(\frac{\omega L}{R}))$$


$$\therefore A = \frac{-V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\alpha - \tan^{-1}(\frac{\omega L}{R}))$$

For transient free response, A must be zero.

$$\therefore \sin(\alpha - \tan^{-1}(\frac{\omega L}{R})) = 0$$

$$\therefore \alpha = \tan^{-1}(\frac{\omega L}{R})$$

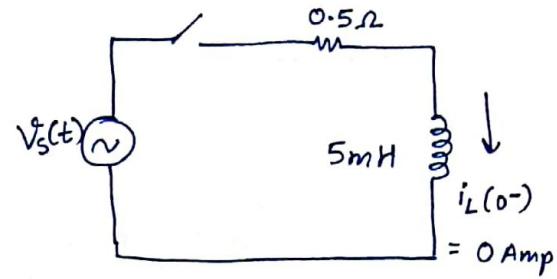For $\omega = 100\pi \text{ rad/s}$, $L = 5 \text{ mH}$, $R = 0.5 \Omega$, we get $\alpha = 1.26 \text{ rad} = 72.34^\circ$



$$\therefore \text{At steady state, } i(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t)$$

$$i(t) = i_{ss} = \frac{100}{\sqrt{(0.5)^2 + (2\pi \times 50 \times 5 \times 10^{-3})^2}} \sin(\omega t)$$

$$\therefore i_{ss} = 200 \sin(2\pi 50t) \text{ A} = 200 \angle 0^\circ \text{ A}$$

ii) Let switching happens at $t=t_0$ so as to avoid transients,

$$\therefore i(t_0^-) = i(t_0^+) = i(t_0) = 0 \text{ and } \alpha = 0 \text{ (given)}$$

\therefore Equation of $i(t)$ can be written as,

$$i(t) = \underbrace{A \cdot e^{-R(t-t_0)/L}}_{\text{Transient factor}} + B \sin(\omega t - \phi)$$

$(t-t_0)$: because 't' is measured after switching | where $B = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}}$, $\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$

If $t=t_0$ and for transient-free response,

$$i(t_0) = \underbrace{0}_{\text{Transient factor}} + B \sin(\omega t_0 - \phi)$$


$$0 = B \sin(\omega t_0 - \phi)$$

$$\therefore \omega t_0 = \phi \Rightarrow t_0 = \frac{\tan^{-1}\left(\frac{\omega L}{R}\right)}{\omega} = \frac{1.26}{2\pi \times 50}$$


$$\underline{t_0 = 4.02 \text{ msec}}$$

Problem ⑤:

(a)

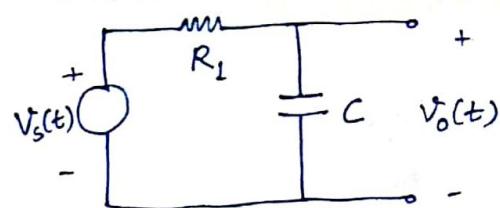
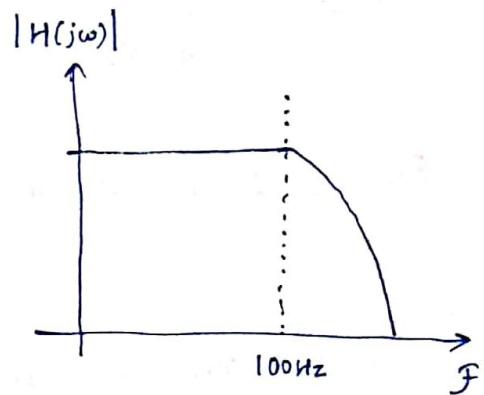
$$V_o = V_s \times \frac{\left(\frac{1}{j\omega C}\right)}{R_1 + \left(\frac{1}{j\omega C}\right)} = \frac{1}{1 + jR_1\omega C}$$



$$\therefore \frac{V_o(j\omega)}{V_s(j\omega)} = \frac{1}{(1 + j\omega R_1 C)}$$

We need a filter with a cut-off frequency of 100Hz as shown above.

If we take $R_1 = 1\text{k}\Omega$, we get $R_1 C = \frac{1}{2\pi \times 100}$


$$\therefore C = \frac{1}{2\pi \times 100 \times R_1} = \frac{1}{2\pi \times 100 \times 10^3} = 1.59 \mu\text{F}$$

$$\therefore \text{Filter transfer function } \Rightarrow H_o(j\omega) = \frac{1}{1 + j(10^3 \times 1.59 \times 10^{-6})\omega} = \frac{1}{(1 + j0.00159\omega)}$$

(b)

If a resistor is connected at output,
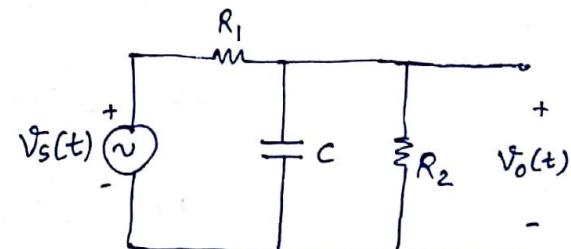
$$\begin{aligned} \frac{V_o}{V_s} &= \frac{\left[R_2 \cdot \left(\frac{1}{j\omega C}\right)\right] / \left[R_2 + \frac{1}{j\omega C}\right]}{R_1 + \frac{\left[R_2 \cdot \frac{1}{j\omega C}\right]}{R_2 + \left(\frac{1}{j\omega C}\right)}} \\ &= \frac{\frac{R_2}{1 + j\omega C R_2}}{R_1 + \frac{R_2}{1 + j\omega C R_2}} \end{aligned}$$



$$\begin{aligned} &= \frac{\frac{R_2}{1 + j\omega C R_2}}{R_1 + \frac{R_2}{1 + j\omega C R_2}} = \frac{R_2}{(R_1 + R_2 + j\omega C R_2 R_1)} \end{aligned}$$

$$\therefore H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)} = \frac{1}{1 + j\omega CR_1 + \left(\frac{R_1}{R_2}\right)}$$

For $R_2 = 200\Omega$ $\Rightarrow H(j\omega) = \frac{1}{(6 + j0.00159\omega)} = \frac{0.166}{1 + j0.00026\omega}$

For $R_2 = 20k\Omega$ $\Rightarrow H(j\omega) = \frac{1}{1.05 + j0.00159\omega} = \frac{0.953}{1 + j0.00159\omega}$

We can see that for $R_2 = 20k\Omega$, $H(j\omega) \approx H_0(j\omega)$.

Steady state output $V_o(t)$ in part @ :

$$V_s(t) = 50 \sin(2\pi 50t + 30^\circ) + 10 \sin(2\pi 500t) \text{ v}$$

$$= V_{s_1}(t) + V_{s_5}(t)$$

Using superposition theorem, for $V_{s_1}(t)$ source, we get,

$$V_{o_1}(t) = \frac{1}{(1 + j0.00159 \times 2\pi \times 50)} \cdot V_{s_1}(t)$$

$\rightarrow \sin(2\pi 50t)$ as reference,

$$\begin{aligned} \bar{V}_{o_1} &= (0.8946 \angle -26.54^\circ) \cdot 50 \angle 30^\circ \\ &= 44.73 \angle 30^\circ - 26.54^\circ \\ &= 44.73 \angle 3.46^\circ \end{aligned}$$

$$\bar{V}_{s_1} = 50 \angle 30^\circ \text{ v}$$

$$\therefore V_{o_1}(t) = 44.73 \sin(2\pi 50t + 3.46^\circ) \text{ v}$$

Similarly, for $V_{s_5}(t)$ source, we get,

$$V_{o_5}(t) = \frac{1}{(1 + j0.00159\omega)} \cdot V_{s_5}(t)$$

Reference: $\sin(2\pi 500t)$

$$\therefore \bar{V}_{s_5} = 10 \angle 0^\circ \text{ v}$$

$$V_{05}(t) = \frac{1}{1 + j(0.00159 \times 2\pi \times 500)} \cdot 10 \angle 0^\circ$$

$$= (0.1963 \angle -78.67^\circ) \times 10 \angle 0^\circ$$

$$= 1.963 \angle -78.67^\circ \text{ V}$$

$$= 1.963 \sin(2\pi 500t - 78.67^\circ) \text{ V}$$

$$\therefore V_o(t) = V_{o1}(t) + V_{o5}(t)$$

$$V_o(t) = 44.73 \sin(2\pi 50t + 3.46^\circ) + 1.963 \sin(2\pi 500t - 78.67^\circ) \text{ Volts.}$$

Problem 10 :

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{\left(\frac{1}{j\omega C} + j\omega L\right)}{R + j\omega L + \frac{1}{j\omega C}}$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\left(\omega L - \frac{1}{\omega C}\right)}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = H(j\omega)$$

$$\text{For } \omega_0 = \frac{1}{\sqrt{LC}} = 1571.3 \text{ rad/s.} \Rightarrow |H(j\omega_0)| = 0$$


For frequencies around ' ω_0 ' \Rightarrow for $\omega < \omega_0 \rightarrow$ we get $\frac{1}{\omega C} > \omega L$

$$\therefore \angle H(j\omega) \approx -90^\circ$$

For $\omega > \omega_0 \rightarrow$ we get, $\frac{1}{\omega C} < \omega L$

$$\angle H(j\omega) \approx 90^\circ$$

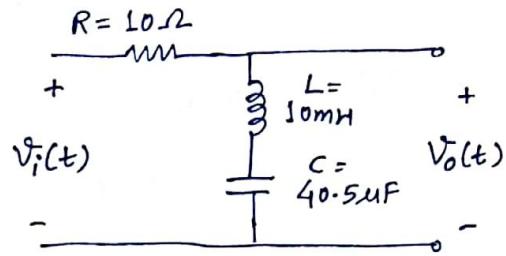For ' ω ' tends to 0 $\Rightarrow \lim_{\omega \rightarrow 0} \angle H(j\omega) = 0^\circ$




$$\angle H(j\omega) =$$

$$90^\circ - \tan^{-1} \left[\frac{\omega^2 LC - 1}{\omega CR} \right]$$

Similarly, $\angle H(j\omega) = 0^\circ$

$\lim: \omega \rightarrow \infty$

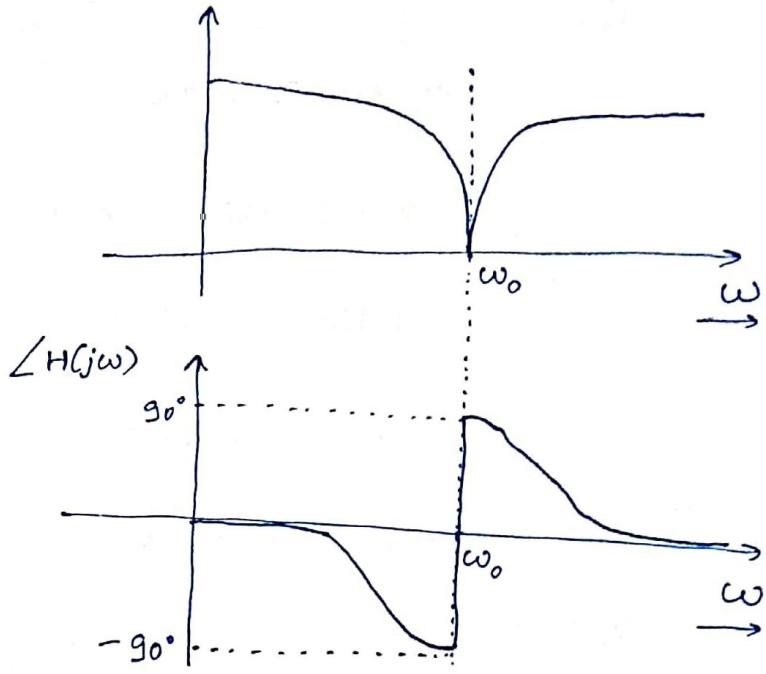\therefore Frequency response \Rightarrow



Output voltage in steady state :

$$\begin{aligned} v_i(t) &= 50 \sin(2\pi \times 50t - 3^\circ) + 10 \sin(2\pi \times 250t) + 5 \sin(2\pi \times 750t + 15^\circ) \text{ V} \\ &= v_{i_1}(t) + v_{i_5}(t) + v_{i_{15}}(t) \end{aligned}$$

Using superposition theorem, for $v_{i_1}(t)$ source,

$$v_{o_1}(t) = \underbrace{j(2\pi \times 50 \times 10 \times 10^3 - \frac{1}{(2\pi \times 50 \times 40.5 \times 10^{-6})})}_{10 + j(2\pi \times 50 \times 10 \times 10^3 - \frac{1}{2\pi \times 50 \times 40.5 \times 10^{-6}})} \times v_s(t)$$

$$\overline{v_{o_1}} = (0.9913 \angle -7.55^\circ) \times 50 \angle -3^\circ$$

$$\overline{v_{o_1}} = 49.566 \angle -10.55^\circ \text{ V}$$

$$v_{o_1}(t) = 49.566 \sin(2\pi \times 50t - 10.55^\circ) \text{ V.}$$

Reference :

$$\sin(2\pi \times 50t)$$

~~$\sin(2\pi \times 50t - 3^\circ)$~~

$$\overline{v_{i_1}} = 50 \angle -3^\circ$$

For $V_{i_5}(t)$ source ,

$$V_{o_5}(t) = \frac{j \left(2\pi \times 250 \times 10 \times 10^{-3} - \frac{1}{2\pi \times 250 \times 40.5 \times 10^{-6}} \right)}{10 + j \left(2\pi \times 250 \times 10 \times 10^{-3} - \frac{1}{(2\pi \times 250 \times 40.5 \times 10^{-6})} \right)} \times V_{i_5}(t)$$

$$\stackrel{?}{=} \left(\frac{1}{10} \right) \times 10 \angle 0^\circ$$

$$\therefore \overline{V_{o_5}} = 1 \angle 0^\circ \text{ v}$$

$$\therefore \overline{V_{o_5}(t)} = \sin(2\pi \times 250 t)$$

For $V_{i_{15}}(t)$ source ,

$$V_{o_{15}}(t) = \frac{j \left[2\pi \times 750 \times 10 \times 10^{-3} - \frac{1}{(2\pi \times 750 \times 40.5 \times 10^{-6})} \right]}{10 + j \left[2\pi \times 750 \times 10 \times 10^{-3} - \frac{1}{2\pi \times 750 \times 40.5 \times 10^{-6}} \right]} \times V_{i_{15}}(t)$$

$$\begin{aligned} &\text{Reference :} \\ &\sin(2\pi \times 750 t) \\ \therefore \overline{V_{o_{15}}} &= 5 \angle 15^\circ \end{aligned}$$

$$\therefore \overline{V_{o_{15}}} = (0.3726 \angle 13.425^\circ) \times 5 \angle 15^\circ \text{ v}$$

$$= 4.8632 \angle 28.43^\circ$$

$$\therefore \overline{V_{o_{15}}(t)} = 4.8632 \sin(2\pi \times 750 t + 28.43^\circ) \text{ v.}$$

\therefore Expression for output voltage,

$$V_o(t) = 49.566 \sin(2\pi 50t - 10.55^\circ) + \sin(2\pi \times 250t) +$$

$$4.8632 \sin(2\pi \times 750t + 28.43^\circ)$$

Problem (1)

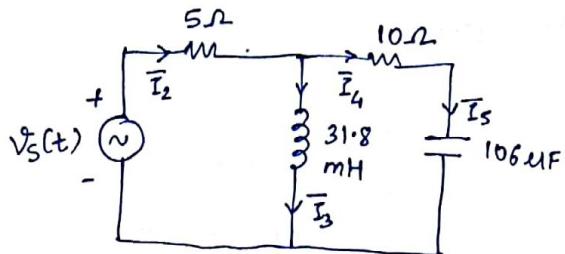


Fig. ①

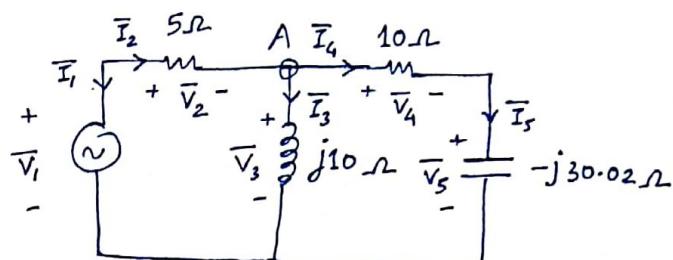


Fig ②

From fig ②, $\bar{V}_1 = \bar{V}_s$

$$\bar{I}_4 = \bar{I}_5$$

$$\bar{I}_1 = -\bar{I}_2$$

$$\bar{V}_s(t) = 100 \sin(2\pi 50t + 30^\circ)$$

Taking reference as $\sin(2\pi 50t)$,

$$\bar{V}_s = 100 \angle 30^\circ V. = \bar{V}_1$$

Applying KCL at Node A,

$$\frac{\bar{V}_3 - \bar{V}_1}{5} + \frac{\bar{V}_3}{(j10)} + \frac{\bar{V}_3}{(10 - j30.02)} = 0$$

$$\frac{\bar{V}_3 - 100 \angle 30^\circ}{5} + \frac{\bar{V}_3}{(j10)} + \frac{\bar{V}_3}{(10 - j30.02)} = 0$$

Solving this gives us, $\bar{V}_3 = 90.35 \angle 48.44^\circ V.$

$$\bar{I}_4 = \bar{I}_5 = \frac{\bar{V}_3}{(10 - j30.02)} = 2.855 \angle 120.01^\circ A, \quad \bar{I}_3 = \frac{\bar{V}_3}{(j10)} = 9.035 \angle -41.56^\circ A$$

$$\bar{V}_4 = (10) \bar{I}_4 = 28.55 \angle 120.01^\circ V, \quad \bar{V}_2 = \bar{V}_1 - \bar{V}_3 = 31.95 \angle -33.43^\circ V$$

$$\bar{V}_5 = (-j30.02) \bar{I}_4 = (30.02 \angle -90^\circ)(2.855 \angle 120.01^\circ) = 85.7 \angle 30.01^\circ V.$$

$$\bar{I}_2 = \frac{\bar{V}_1 - \bar{V}_3}{5} = 6.39 \angle -33.43^\circ A, \quad \bar{I}_1 = -\bar{I}_2 = 6.39 \angle 146.57^\circ A$$

$$\begin{aligned}
 & \sum_{k=1}^5 V_k I_k^* \\
 &= V_1 I_1^* + V_2 I_2^* + V_3 I_3^* + V_4 I_4^* + V_5 I_5^* \\
 &= (100 \angle 30^\circ) (6.39 \angle -146.57^\circ) \cancel{(2.855 \angle 167.57^\circ)} \\
 &= (100 \angle 30^\circ) (6.39 \angle -146.57^\circ) + (31.95 \angle -33.43^\circ) (6.39 \angle 33.43^\circ) + \\
 &\quad (90.35 \angle 48.44^\circ) (9.035 \angle 41.56^\circ) + (28.55 \angle 120.01^\circ) (2.855 \angle -120.01^\circ) \\
 &\quad + (85.7 \angle 30.01^\circ) (2.855 \angle -120.01^\circ) \\
 &= 0
 \end{aligned}$$

$$\therefore \sum_{k=1}^5 V_k I_k^* = 0$$

Problem 12: $V_s(t) = 5 + 10 \sin(2\pi \times 50t + 30^\circ) + 3 \sin(2\pi \times 150t - 60^\circ)$

+ $0.5 \sin(2\pi \times 300t)$ volt.

$$= V_{dc} + V_1(t) + V_3(t) + V_6(t)$$

Using superposition theorem,

For V_{dc} source, $i_{dc} = \frac{5}{10} = 0.5 \text{ Amp.}$

For $V_1(t)$ source, $i_1(t) = \frac{10}{\sqrt{8(10)^2 + (2\pi \times 50 \times 16 \times 10^{-3})^2}} \cdot \sin [2\pi 50t + 30^\circ - \tan^{-1} \left(\frac{2\pi 50 \times 16 \times 10^{-3}}{10} \right)]$

$$\therefore i_1(t) = 0.893 \sin(2\pi 50t + 30^\circ - 26.686^\circ)$$

$$i_1(t) = 0.893 \sin(2\pi 50t + 3.31^\circ) \text{ A.}$$

For $V_3(t)$ source ,

$$i_3(t) = \frac{3}{\sqrt{(10)^2 + (2\pi \times 150 \times 16 \times 10^{-3})^2}} \sin \left[2\pi \times 150t - 60 - \tan^{-1} \left(\frac{2\pi \times 150 \times 16 \times 10^{-3}}{10} \right) \right]$$

$$i_3(t) = 0.166 \sin(2\pi \times 150t - 116.45^\circ) \text{ Amp.}$$

For $V_6(t)$ source ,

$$i_6(t) = \frac{0.5}{\sqrt{(10)^2 + (2\pi \times 300 \times 16 \times 10^{-3})^2}} \sin \left[2\pi \times 300t - \tan^{-1} \left(\frac{2\pi \times 300 \times 16 \times 10^{-3}}{10} \right) \right]$$

$$i_6(t) = 0.0157 \sin(2\pi \times 300t - 71.655^\circ) \text{ Amp.}$$

$$\text{Power dissipated across resistor} = I_{\text{rms}}^2 \cdot R$$

For each Component of Current , we can find power dissipated as ,

$$P_{dc} = I_{dc}^2 \cdot R = (0.5)^2 \times 10 = 2.5 \text{ W}$$

$$\text{Due to } i_1(t) \Rightarrow P_1 = I_{1\text{rms}}^2 R = \left(\frac{0.893}{\sqrt{2}} \right)^2 \times 10 = 3.98 \text{ W}$$


$$\text{Due to } i_3(t) \Rightarrow P_3 = \left(\frac{0.166}{\sqrt{2}} \right)^2 \times 10 = 0.13778 \text{ W}$$

$$\text{Due to } i_6(t) \Rightarrow P_6 = \left(\frac{0.0157}{\sqrt{2}} \right)^2 \times 10 = 0.00123 \text{ W}$$

$$\begin{aligned} \therefore \text{Total power dissipated across resistor} &= 2.5 + 3.98 + 0.13778 + 0.00123 \\ &= 6.62 \text{ Watts.} \end{aligned}$$

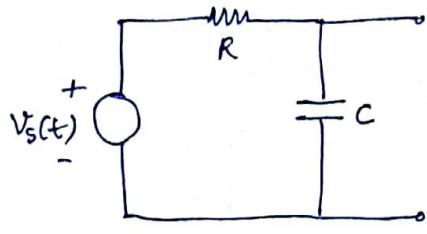Problem 13 :

$$\frac{V_o}{V_s} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$



$$\frac{V_o}{V_s} = \frac{1}{(1+j\omega RC)} \Rightarrow H(j\omega) = \frac{1}{1+j\omega RC} = \frac{1}{\sqrt{1+(\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$

From Fourier Series of $V_s(t)$, we can write,

$$V_s(t) = a_0 + \sum_{n \in \mathbb{Z}^+} a_n \sin(n\omega t) + \sum_{n \in \mathbb{Z}^+} b_n \cos(n\omega t)$$

By looking at waveform of $V_s(t)$, we can say that it has zero average value.

$$\therefore a_0 = 0$$

$V_s(t)$ is also an 'odd' function, $\therefore b_n = 0$ for all values of 'n'.

$V_s(t)$ satisfies half wave symmetry, i.e. $V_s(t + T/2) = -V_s(t - T/2)$

$$\therefore a_n = 0 \text{ for } n = 2, 4, 6, 8, \dots$$

$$\therefore V_s(t) = \sum_{n=1,3,5\dots} a_n \sin(n\omega t) \quad \text{where } \omega = 2\pi \times 100 \text{ rad/sec.}$$

$$a_n = \frac{1}{T/2} \int_0^{T/2} V_s(t) \sin(n\omega t) dt = \frac{4V}{n\pi} \quad \text{where } V = 10$$

$$\therefore a_n = \frac{40}{n\pi}$$

$$\therefore V_s(t) = \sum_{n=1,3,5\dots} \left(\frac{40}{n\pi} \right) \sin(n\omega t)$$

$$\frac{V_o}{V_s} = \frac{1}{1+j\omega RC} \Rightarrow \cancel{V_o} = \cancel{\left(\frac{40}{n\pi} \right) \times \cancel{1}}$$

$$\therefore V_o(t) = \sum_{n=1,3,5\ldots} \left(\frac{40}{n\pi} \right) \frac{1}{\sqrt{n^2\omega^2 R^2 C^2 + 1}} \cdot \sin[n\omega t - \tan^{-1}(n\omega RC)]$$

Frequency response


$$\text{of } \frac{V_o}{V_s} = \frac{1}{1+j\omega RC}$$

For $C = 0.25 \mu F$:

From frequency response of

$H(j\omega)$, we can see that

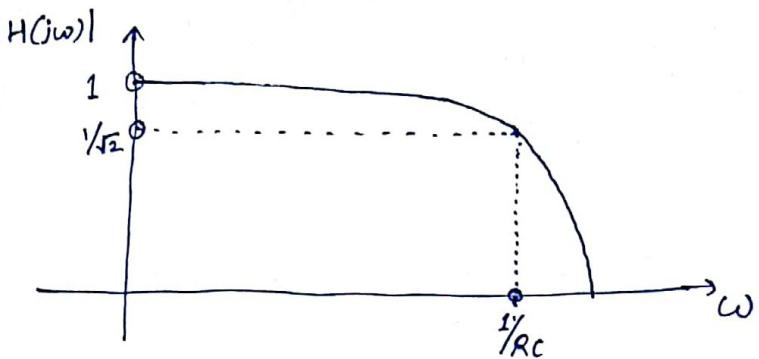
it acts as a low pass filter
with cut off frequency of
 636.62 Hz .



$$\omega_c = 1/\sqrt{RC}$$


$$= 636.62 \text{ Hz}$$

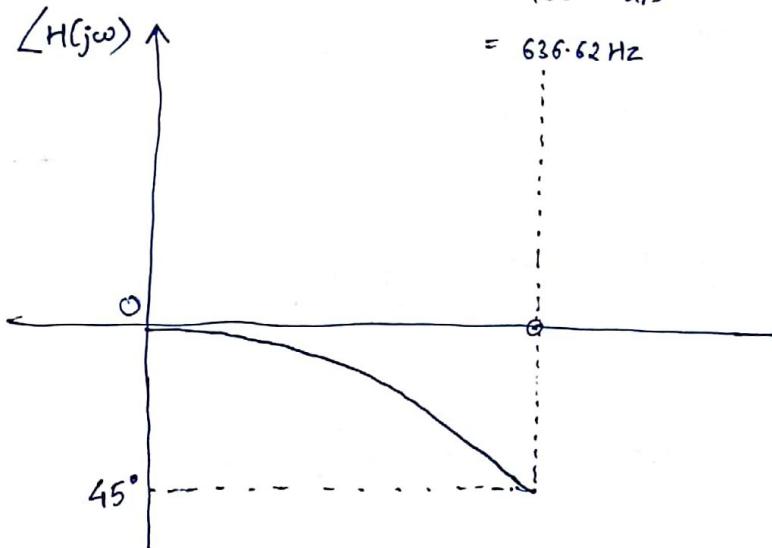$\therefore V_o(t)$ will dominantly
consists of frequency components
upto 636 Hz . (since filter is
not ideal, frequency components
above 636 Hz will also be present, but they will not be as dominant).



$\therefore V_o(t)$ will dominantly consist of 1st, 3rd and 5th harmonic (i.e., 100Hz, 300Hz and 500Hz).

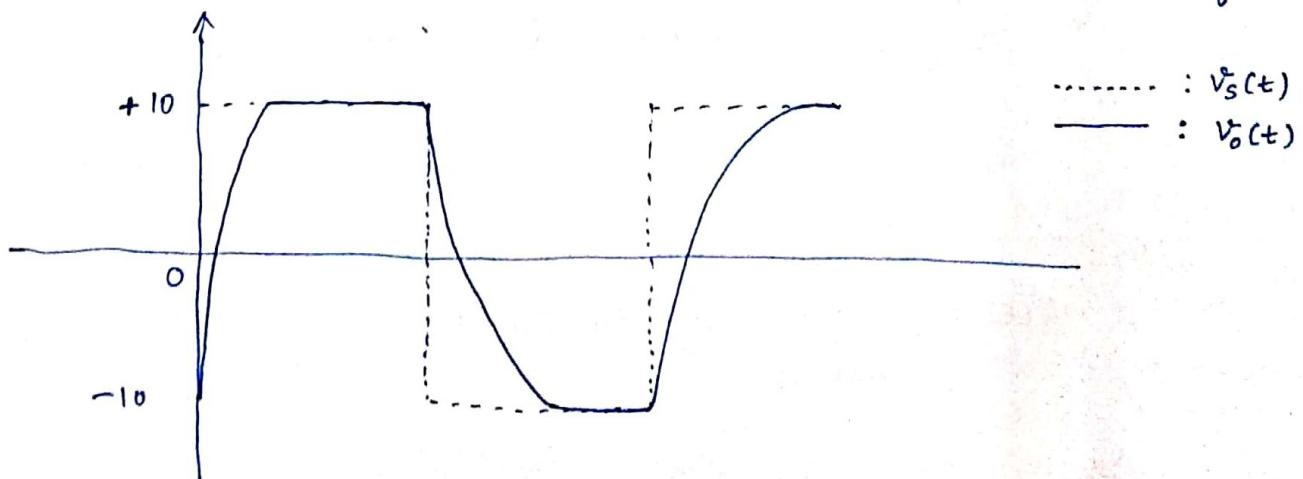so the waveform of $V_o(t)$ will be closer to sinusoidal as compared to that of $V_s(t)$.



..... : $V_s(t)$
— : $V_o(t)$

For $C = 50\mu F$,

$$\frac{V_o}{V_s} = \frac{1}{1 + j0.05\omega}$$

$$\omega RC = (\omega \times 10^3 \times 50 \times 10^{-6})$$

$$= 0.05\omega$$

$$\text{For } 100\text{Hz}, \quad \omega RC = 31.41$$


$$\therefore \text{For significant frequencies, we can write } \frac{V_o}{V_s} \approx \frac{1}{j(\omega 0.05)}$$

$$\therefore V_o = \frac{V_s}{j\omega \times 0.05}$$


— : $V_s(t)$

$$\therefore V_o(t) \approx \frac{1}{RC} \int V_s(r) dr$$

- - - : $V_o(t)$

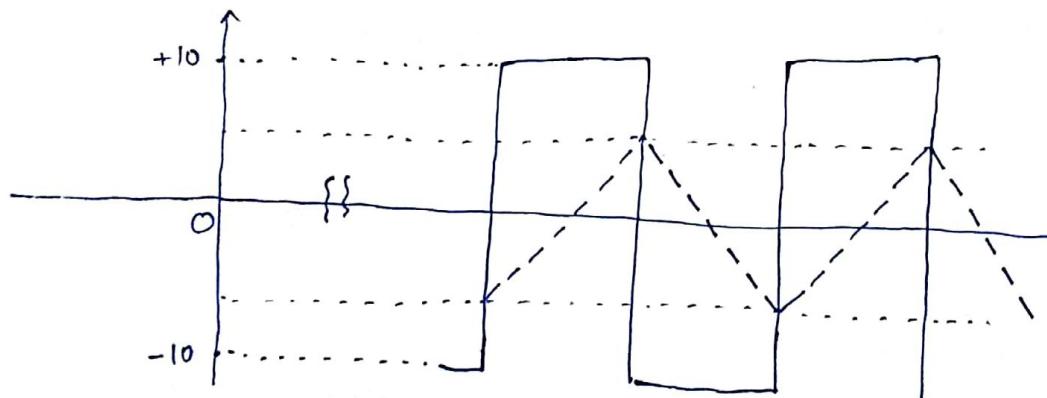

Problem 14 :

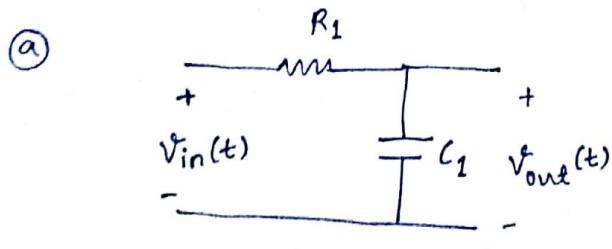

$$\text{Transfer Function} : \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}}$$

$$\therefore \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + sR_1C_1}$$

$$\text{Gain} = \left| \frac{V_{\text{out}}(j\omega)}{V_{\text{in}}(j\omega)} \right| = \left| \frac{1}{1 + j\omega R_1 C_1} \right| = \frac{1}{\sqrt{\omega^2 R_1^2 C_1^2 + 1}}$$

At low frequencies ($\omega \rightarrow 0$) \Rightarrow we have $G_1 \approx 1$

At high frequencies ($\omega \rightarrow \infty$) $\Rightarrow G_1 \approx 0$

\Rightarrow If $\omega \gg R_1 C_1$, then it is called High frequencies.

If $\omega \ll R_1 C_1 \Rightarrow$ they are called as Low frequencies.

$$\Rightarrow \text{Gain } (G_1) = \frac{1}{\sqrt{1 + \omega^2 R_1^2 C_1^2}}$$


$$\frac{dG_1}{d\omega} = \frac{\omega R_1^2 C_1^2}{(1 + \omega^2 R_1^2 C_1^2)^{3/2}}$$

$$\Rightarrow \text{At high frequencies } (\text{i.e. } \omega \rightarrow \infty) \quad \frac{dG_1}{d\omega} = \frac{\omega R_1^2 C_1^2}{\omega^3 R_1^3 C_1^3}$$

$$(\omega^2 R_1^2 C_1^2 \gg 1)$$

$$\therefore \frac{dG_1}{d\omega} \propto \frac{1}{\omega^2} \quad \text{at high frequencies.}$$

(b)

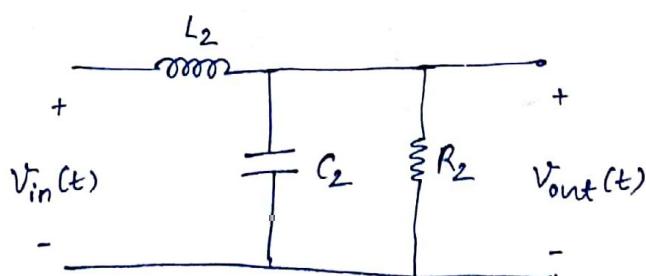

$$\begin{aligned} \text{Transfer Function} &= \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} \\ &= \frac{\left(\frac{1}{sC_2} \right) || (R_2)}{sL_2 + \left[\left(\frac{1}{sC_2} \right) || R_2 \right]} \end{aligned}$$

$$= \frac{R_2}{s^2 R_2 L_2 C_2 + s R_2 C_2 + R_2}$$

$$\therefore \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = \frac{1}{s^2 L_2 C_2 + s C_2 + 1}$$

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = \frac{\left(\frac{1}{L_2 C_2}\right)}{s^2 + \frac{s}{L_2} + \frac{1}{L_2 C_2}}$$

$$G_{in} = \left| \frac{V_{out}(j\omega)}{V_{in}(j\omega)} \right| = \left| \frac{\frac{1}{L_2 C_2}}{\omega^2 + \left(\frac{1}{L_2 C_2}\right) j + \left(\frac{1}{L_2 C_2}\right)} \right|$$

$$\therefore G_2 = \frac{1}{\sqrt{(1 - \omega^2 L_2 C_2)^2 + \omega^2 L_2^2}}$$

At low frequencies $\Rightarrow \omega \rightarrow 0 \Rightarrow G_2 \approx 1$

At high frequencies $\Rightarrow \omega \rightarrow \infty \Rightarrow G_2 \approx 0$

\therefore If $\omega > \frac{1}{\sqrt{L_2 C_2}}$ \Rightarrow then it is called high frequencies

If $\omega \ll \frac{1}{\sqrt{L_2 C_2}}$ \Rightarrow then it is called as Low frequencies.

$$\frac{dG_2}{d\omega} = \frac{d}{d\omega} \left| \frac{1}{(\omega^4 L_2^2 C_2^2 + \omega^2 (C_2^2 - 2L_2 C_2) + 1)^{1/2}} \right|$$

Take $a = L_2^2 C_2^2$ & $b = C_2^2 - 2L_2 C_2$

$$\therefore \frac{dG_2}{d\omega} = \frac{d}{d\omega} \left| \frac{1}{(a\omega^4 + b\omega^2 + 1)^{1/2}} \right|$$

$$\therefore \frac{dG_2}{d\omega} = \frac{2a\omega^3 + bw}{(aw^4 + bw^2 + 1)^{3/2}}$$

∴ At high frequencies, $\frac{dG_1}{d\omega} \propto \frac{1}{\omega^3}$

⇒ So, $\frac{dG_1}{d\omega} \propto \frac{1}{\omega^2}$ and $\frac{dG_2}{d\omega} \propto \frac{1}{\omega^3}$

∴ Filter in part ① has lower gain at high frequencies as compared to filter in part ②. ∴ ~~Filter~~ Filter in part ① is better than that in Part ②.

2

(t).