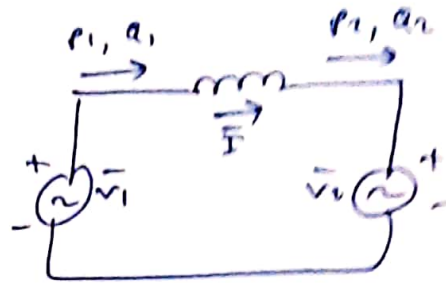


Q-1

(a)

$$\bar{V}_1 = V_1 \angle \delta_1$$

$$\bar{V}_2 = V_2 \angle \delta_2$$



$$\bar{I} = \frac{\bar{V}_1 - \bar{V}_2}{jX}$$

$$\begin{aligned} \rightarrow P_1 + jQ_1 &= \bar{V}_1 \bar{I}^* \\ &= V_1 \angle \delta_1 \left[\frac{V_1 \angle -\delta_1 - V_2 \angle -\delta_2}{X \angle -90^\circ} \right] \end{aligned}$$

$$\therefore P_1 = \frac{V_1 V_2}{X} \sin(\delta_1 - \delta_2)$$

$$Q_1 = \frac{V_1^2}{X} - \frac{V_1 V_2}{X} \cos(\delta_1 - \delta_2)$$

$$\begin{aligned} \rightarrow P_2 + jQ_2 &= \bar{V}_2 \bar{I}^* \\ &= V_2 \angle \delta_2 \left[\frac{V_1 \angle -\delta_1 - V_2 \angle -\delta_2}{X \angle -90^\circ} \right] \end{aligned}$$

$$\therefore P_2 = \frac{V_1 V_2}{X} \sin(\delta_1 - \delta_2)$$


$$Q_2 = \frac{V_1 V_2}{X} \cos(\delta_2 - \delta_1) - \frac{V_2^2}{X}$$

(b) If $\delta_1 > \delta_2 \Rightarrow P_1 > 0$ & $P_2 > 0$

\therefore Active power flow from source 1 to source 2.

$$\underline{(c)} \quad P_{\max} = \frac{V_1 V_2}{X} = \frac{400 \times 400}{50} = 3200 \text{ MW}$$

(d)

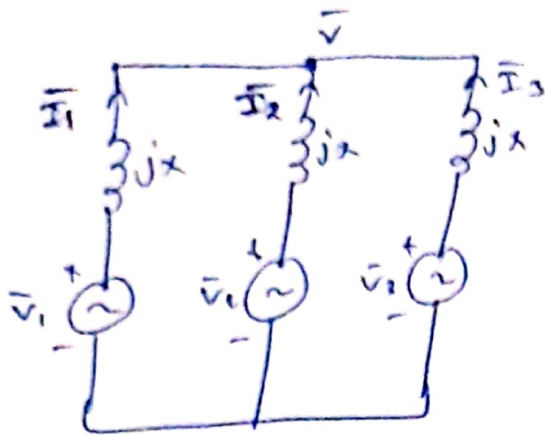

→ KVL eqⁿs

$$\bar{v}_1 - jx\bar{I}_1 + jx\bar{I}_2 - \bar{v}_2 = 0$$

$$\bar{v}_2 - jx\bar{I}_2 + jx\bar{I}_3 - \bar{v}_3 = 0$$

→ KCL eqⁿ

$$\bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 0$$

$$\therefore \bar{V} = \frac{\bar{v}_1 + \bar{v}_2 + \bar{v}_3}{3} = 234.18 \angle -3.2227^\circ$$

$$\therefore P_1 > 0, P_2 > 0 \text{ \& } P_3 < 0$$

(e)

To reduce the capacitor voltage read power should flow from AC side ^{of inverter} to ~~source~~ grid. So, first we have to make δ positive until capacitor voltage reduce to its desire value and then we have to make $\delta = 0$ to stop further reduction of capacitor voltage.

→ Ans → (b) Make δ positive and return to its original value.

Q-2

Under steady state condition ($s \rightarrow 0$)

$$\frac{1 + sT_1}{1 + sT_2} \Rightarrow 1$$

$$\frac{1}{1 + sT_F} \rightarrow 1$$

$$K \frac{sT}{1 + sT} \rightarrow 0$$

$$K_P + \frac{K_I}{s} \rightarrow \infty$$

$$\rightarrow \therefore A_1 = 0 \text{ \& } A_5 = 0$$

$$\text{Also, } A_2 = A_3 = A_4$$

$$\rightarrow \text{Now, } A_1 = -A_5 - A_4 + J_{ref}$$

$$\therefore A_4 = J_{ref} = 1$$

$$\therefore A_2 = A_3 = 1$$

Q-3

\rightarrow Initial output $y(t=0) = 0$, when $u(t)$ become 1, input to the limiter is 1 and it will clip the limiter output to 2. So, initially output $y(t)$ will rise slowly (with $\tau = 10 \text{ s}$) until it ~~be~~ reaches the value of 0.8. When $y(t) = 0.8$, input to limiter is 2, and after that $y(t)$ very quickly reaches to its steady-state value of $\frac{50}{51}$ (with $\tau = 0.2 \text{ s}$)

→ when $x(t)$ again become zero, input to limiter is less than (-2) , and it will clip the output of the limiter by (-2) . And $y(t)$ starts ~~de~~ reducing (with $\tau = 10$ s). Once input to limiter become greater than (-2) , $y(t)$ very quickly reduces to zero (with $\tau = 0.2$ s)

⇒ Option (A), wrong - $y(t)$ increase very quickly (with $\tau = 0.2$ s)

Option (B), correct option

Option (C), wrong - Incorrect steady-state value.

Option (D), wrong - no delay is applicable

Option (E), wrong - no delay is applicable
output should change immediately after change in $x(t)$.

Option (F), wrong - Incorrect steady-state value.

Q-4

(a)

KVL eqⁿs

$$\bar{V}_{an} - j \bar{I}_a (x_L - x_C) + j \bar{I}_b (x_L - x_C) - \bar{V}_{bn} = 0$$

$$\bar{V}_{bn} - j \bar{I}_b (x_L - x_C) + j \bar{I}_c (x_L - x_C) - \bar{V}_{cn} = 0$$

KCL eqⁿ

$$\bar{I}_a + \bar{I}_b + \bar{I}_c = 0 \quad (\because \text{under balanced condition})$$

$$\bar{I}_a = 0$$

$$\therefore \bar{V}_{ng} = - \left(\frac{\bar{V}_{an} + \bar{V}_{bn} + \bar{V}_{cn}}{3} \right)$$

$$\therefore \boxed{\bar{V}_{ng} = 0 \text{ V}} \quad (\text{as source is balanced})$$

(b) When line-to-ground fault happens on phase 'a', potential diffⁿ betⁿ point 'a' and 'g' is approx. zero. (because $\omega L \ll \frac{1}{\omega C}$)

$$\therefore \bar{V}_{ag} \approx 0$$

$$\rightarrow \text{Now, } \bar{V}_{an} - \bar{V}_{ag} + \bar{V}_{bg} - \bar{V}_{bn} = 0$$


$$\therefore \bar{V}_{bg} \approx \bar{V}_{bn} - \bar{V}_{an} \\ = \sqrt{3} \times 250 \angle -150^\circ \text{ V}$$

$$\rightarrow \bar{V}_{an} - \bar{V}_{ag} + \bar{V}_{cg} - \bar{V}_{cn} = 0$$

$$\therefore \bar{V}_{cg} \approx \bar{V}_{cn} - \bar{V}_{an} \\ = \sqrt{3} \times 250 \angle 150^\circ \text{ V}$$

$\rightarrow \bar{I}_g = 0$, because no closed path is available.

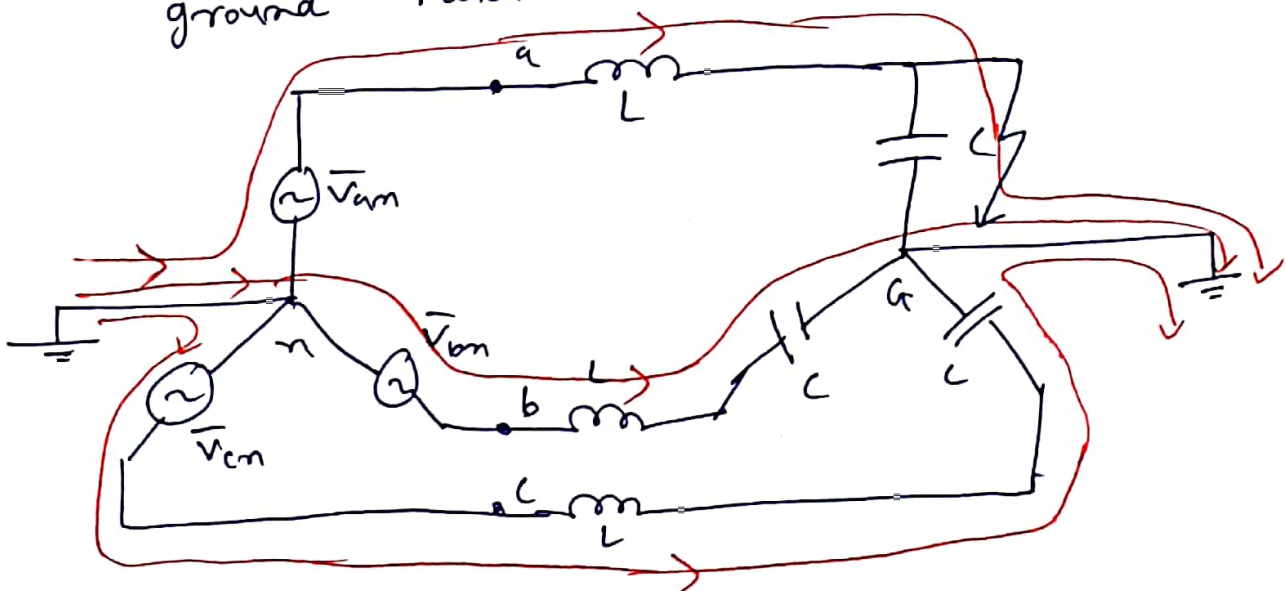(c) When neutral is also grounded and ground resistance is neglected.



$$\rightarrow \bar{V}_{an} - j\omega L \bar{I}_a = 0$$

$$\therefore \bar{I}_a = \frac{\bar{V}_{an}}{j\omega L} = \frac{250}{2 \times \pi \times 50 \times 30 \times 10^{-6}} \angle 90^\circ$$

$$\bar{I}_a = 26.525 \angle -90^\circ \text{ kA}$$

$$\& \bar{V}_{a\phi} = \bar{V}_{an} = 250 \angle 0^\circ \text{ V}$$

$$\rightarrow \bar{V}_{bn} - j\left(\omega L - \frac{1}{\omega C}\right) \bar{I}_b = 0$$

$$\therefore \bar{I}_b = \frac{\bar{V}_{bn}}{j\left(\omega L - \frac{1}{\omega C}\right)} = 4.998 \angle -210^\circ \mu\text{A}$$

$$\& \bar{V}_{b\phi} = \bar{V}_{bn} = 250 \angle -120^\circ \text{ V}$$

$$\rightarrow \bar{V}_{cn} - j\left(\omega L - \frac{1}{\omega C}\right) \bar{I}_c = 0$$

$$\therefore \bar{I}_c = \frac{\bar{V}_{cn}}{j\left(\omega L - \frac{1}{\omega C}\right)} = 4.998 \angle 30^\circ \mu\text{A}$$

$$\& \bar{V}_{c\phi} = \bar{V}_{cn} = 250 \angle 120^\circ \text{ V}$$

$$\rightarrow \bar{I}_\phi = \bar{I}_a + \bar{I}_b + \bar{I}_c = 26.525 \angle -90^\circ \text{ kA}$$

Q-5

In all the three cases, because of the balanced load, the stator current and stator flux is balanced.

→ Balanced stator flux produce stator field rotating at synchronous speed. Also rotor field

is rotating at synchronous speed.

→ So, Net electro-magnetic torque is constant in all the cases. (in steady state).

⇒ Case - (1)

Because of no resistance is present in this load. Active power of the load is zero. And so, ~~torque~~ torque is zero (constant).

⇒ Case - (2), (3)

→ In both cases because of resistance, it will absorb active power. (passive load and generator convention of torque)
→ So, net electro-magnetic torque is constant positive value

Q - 7

Following informations can be extracted from the observations.

- (i) Thevenin impedance have inductive nature.
- (ii) } Thevenin impedance is non-zero (non-ideal)
- (iii) }
- (iv) Efd & field voltage (under open ckt)
- (v) Thevenin impedance does not have resistance.

⇒ From the above information option (A) is correct. All other options does not have inductive thevenin impedance.

Q-8

(a), (b)

→ Under-steady state condition ($s \rightarrow 0$)

$$\therefore \frac{1}{s} \rightarrow \infty \Rightarrow \text{Net torque} = 0 = \frac{P_m - P_e}{\omega}$$

$$\therefore \boxed{P_m = P_e = 60} \text{ mW}$$

$$\rightarrow \text{Also, } \frac{100}{1+0.5s} \rightarrow 100$$

$$\therefore \text{Normalised gate position} = \frac{60}{100} = 0.6$$

$$\rightarrow \text{Governor output} = 0.6 - 0.8 = -0.2$$

$$\therefore \text{Governor input} = \frac{-0.2}{0.25} = -0.8$$

$$\rightarrow \omega_{ref} - \omega = -0.8$$

$$\therefore \omega = \omega_{ref} + 0.8$$
$$= 314.96 \text{ rad}$$

$$\therefore \boxed{\omega = 50.127 \text{ Hz}}$$

(c) Under steady state condition ($s \rightarrow 0$)

$$\therefore \frac{1}{s} \rightarrow \infty \text{ \& } \frac{100}{1+0.5s} \rightarrow 100$$

$$\therefore \boxed{P_e = P_m = 60} \text{ mW}$$

$$\& \text{ Governor output} = -0.2$$

$$\rightarrow \text{But Governor} = (\cancel{0.25} + \frac{0.5}{s}) \rightarrow \infty$$


$$\therefore \text{Governor input} = 0$$

$$\therefore \omega_{ref} - \omega = 0$$

$$\therefore \omega = \omega_{ref} = 314.16 \text{ rad}$$

$$\therefore \boxed{\omega = 50 \text{ Hz}}$$

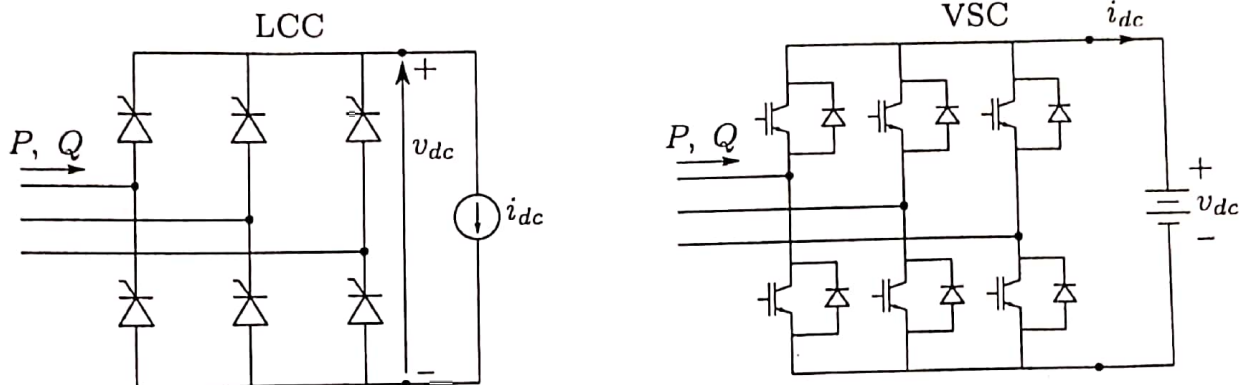6. Consider an LCC and a VSC based device with the directions of v_{dc} , i_{dc} , P and Q for each of them are as shown in the figure below.



For each of the following statements, choose the correct option (for both LCC and VSC).

7 marks

Sl. No.	Statement	LCC	VSC
(i)	Instantaneous i_{dc} can be both positive and negative	True /False	True/ False
(ii)	Average i_{dc} can be both positive and negative	True /False	True/ False
(iii)	Instantaneous v_{dc} can be both positive and negative	True/ False	True /False
(iv)	Average v_{dc} can be both positive and negative	True/ False	True /False
(v)	Active power (P) can be both positive and negative	True/ False	True/ False
(vi)	Reactive power (Q) can be both positive and negative	True /False	True/ False
(vii)	Can feed a purely passive load on the AC side	True /False	True/ False