

EE 334
Response of LTI Circuits to AC and DC Inputs

Prof. A. M. Kulkarni

Electrical Engineering Dept.
IITB, Mumbai




January, 2020

1. Phasors with sine as reference

Considering peak value ...


Time-domain circuit

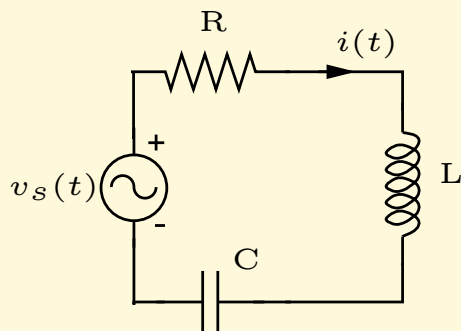

$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

$$R = 10 \, \Omega, L = 0.05 \text{ H}, C = 100 \, \mu\text{F}$$

Phasor equivalent circuit

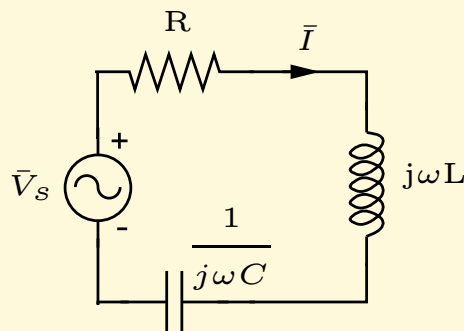

$$\rightarrow \bar{V}_s = 100 \angle 0^\circ \text{ V}$$

Applying KVL:

$$\bar{I} = \frac{\bar{V}_s}{\left(R + j\omega L + \frac{1}{j\omega C}\right)}$$


$$i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A} \quad \leftarrow \quad \bar{I} = 5.27 \angle 58.2^\circ \text{ A}$$

This is sinusoidal steady-state solution.

2. Phasors with **cosine** as reference

Considering peak value ...

Time-domain circuit

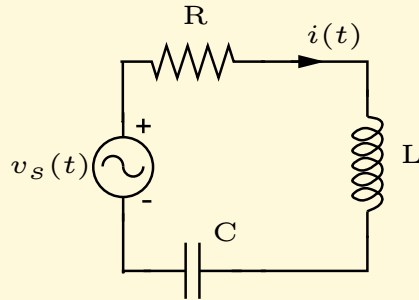


$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

Or $v_s(t) = 100 \cos(2\pi 50t - 90^\circ) \text{ V}$

$$R = 10 \, \Omega, L = 0.05 \text{ H}, C = 100 \, \mu\text{F}$$

Phasor equivalent circuit

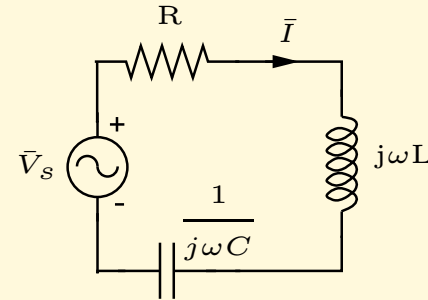

$$\rightarrow \bar{V}_s = 100 \angle -90^\circ \text{ V}$$

Applying KVL:

$$\bar{I} = \frac{\bar{V}_s}{\left(R + j\omega L + \frac{1}{j\omega C} \right)}$$

$$i(t) = 5.27 \cos(2\pi 50t - 31.8^\circ) \text{ A} \quad \leftarrow \quad \bar{I} = 5.27 \angle -31.8^\circ \text{ A}$$


Or $i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A}$

This is sinusoidal steady-state solution.

3. Phasors with **cosine** as reference

Considering RMS value ...

Time-domain circuit

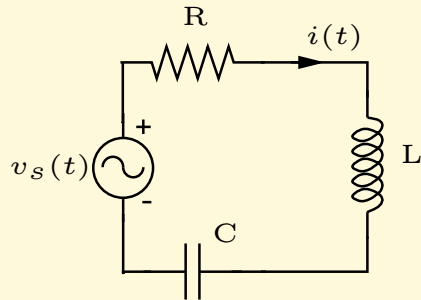


$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

$$\text{Or } v_s(t) = 100 \cos(2\pi 50t - 90^\circ) \text{ V}$$

$$R = 10 \, \Omega, L = 0.05 \text{ H}, C = 100 \, \mu\text{F}$$

Phasor equivalent circuit

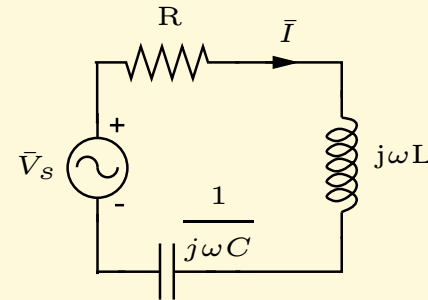

$$\rightarrow \bar{V}_s = 70.71 \angle -90^\circ \text{ V}$$

Applying KVL:

$$\bar{I} = \frac{\bar{V}_s}{\left(R + j\omega L + \frac{1}{j\omega C}\right)}$$

$$i(t) = 5.27 \cos(2\pi 50t - 31.8^\circ) \text{ A} \quad \leftarrow \quad \bar{I} = 3.727 \angle -31.8^\circ \text{ A}$$


$$\text{Or } i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A}$$

This is sinusoidal steady-state solution.

4. Phasors with sine as reference

Considering RMS value ...


Time-domain circuit

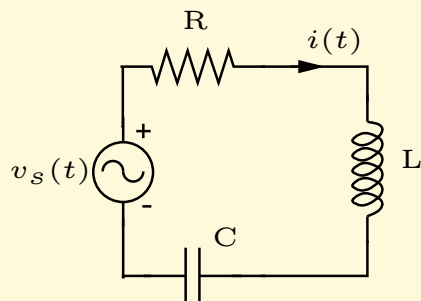

$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

$$R = 10 \, \Omega, L = 0.05 \text{ H}, C = 100 \, \mu\text{F}$$

Phasor equivalent circuit

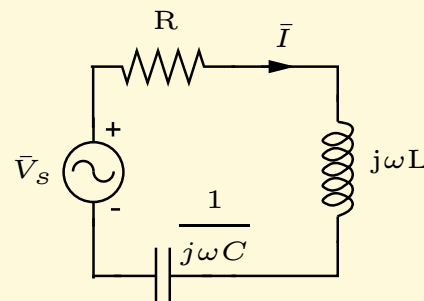

$$\rightarrow \bar{V}_s = 70.71 \angle 0^\circ \text{ V}$$

Applying KVL:


$$\bar{I} = \frac{\bar{V}_s}{\left(R + j\omega L + \frac{1}{j\omega C}\right)}$$

$$i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A} \leftarrow \bar{I} = 3.727 \angle 58.2^\circ \text{ A}$$

This is sinusoidal steady-state solution.

Phasors with **sine** as reference


Time-domain circuit

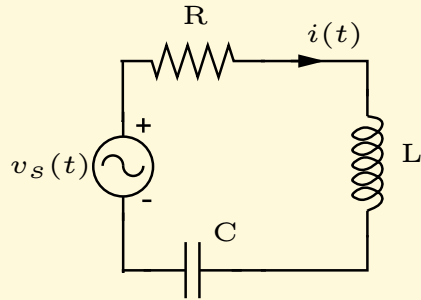

$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

$$i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A}$$


Phasor equivalent circuit

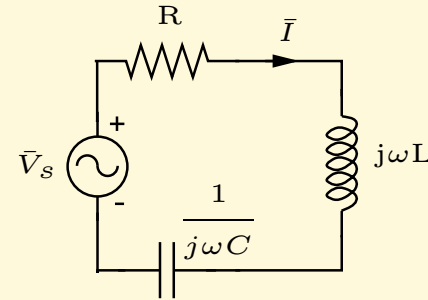

$$\rightarrow \bar{V}_s = 70.71 \angle 0^\circ \text{ V}$$


$$\rightarrow \bar{I} = 3.727 \angle 58.2^\circ \text{ A}$$

Phasor Diagram

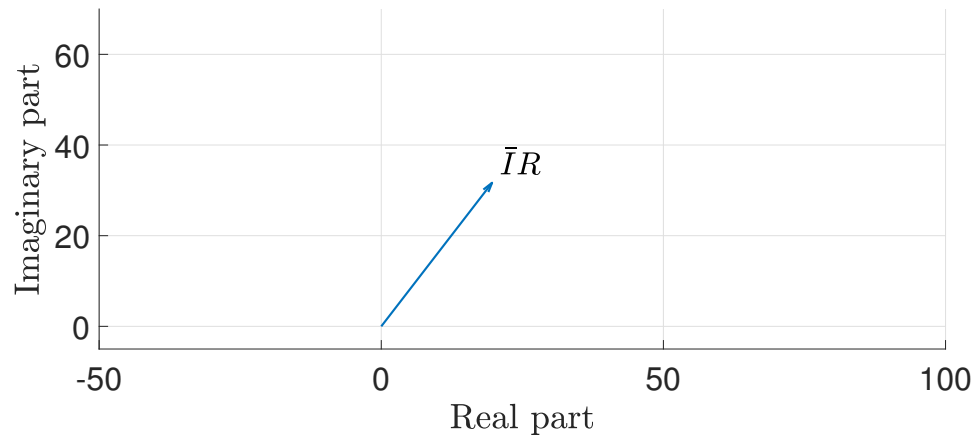

Phasors with **sine** as reference


Time-domain circuit

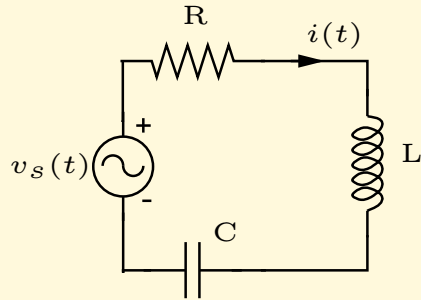

$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

$$i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A}$$


Phasor equivalent circuit

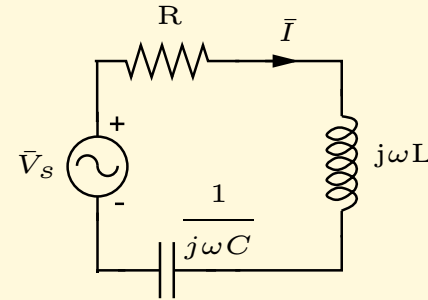

$$\rightarrow \bar{V}_s = 70.71 \angle 0^\circ \text{ V}$$


$$\rightarrow \bar{I} = 3.727 \angle 58.2^\circ \text{ A}$$

Phasor Diagram

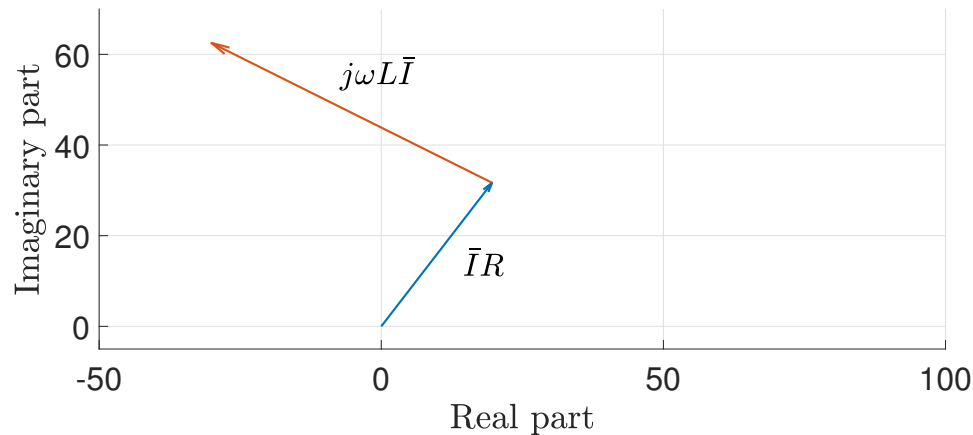

Phasors with **sine** as reference


Time-domain circuit

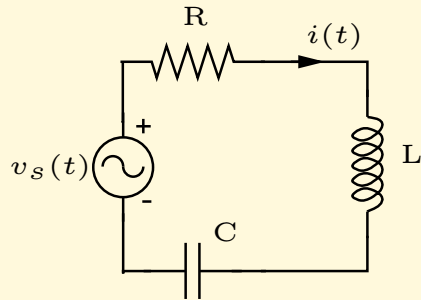

$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$


$$i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A}$$

Phasor equivalent circuit

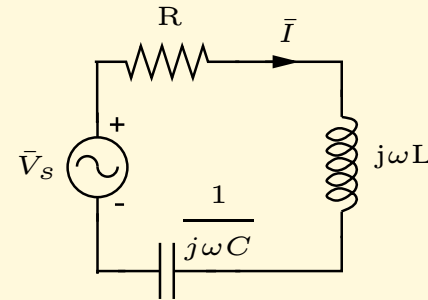


$$\rightarrow \bar{V}_s = 70.71 \angle 0^\circ \text{ V}$$
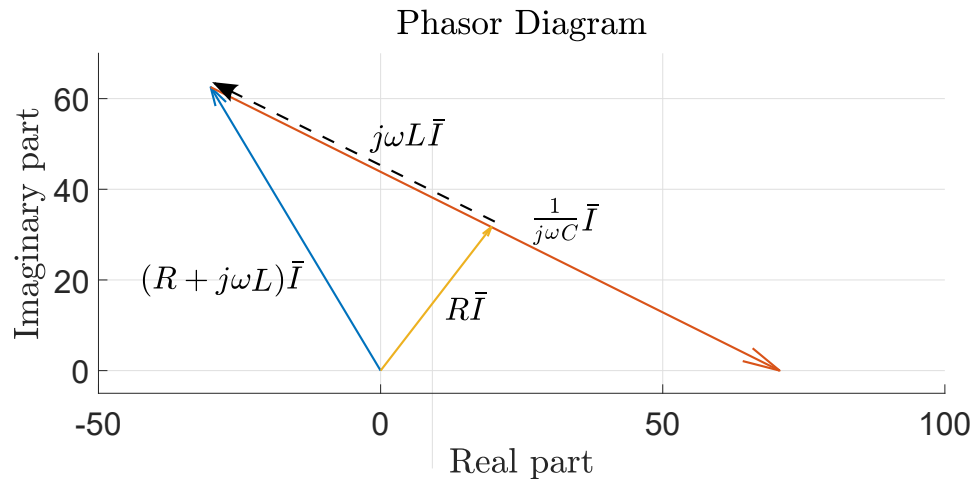
$$\rightarrow \bar{I} = 3.727 \angle 58.2^\circ \text{ A}$$




Phasors with **sine** as reference

Time-domain circuit

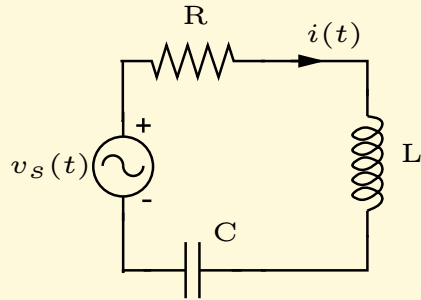

Phasor equivalent circuit

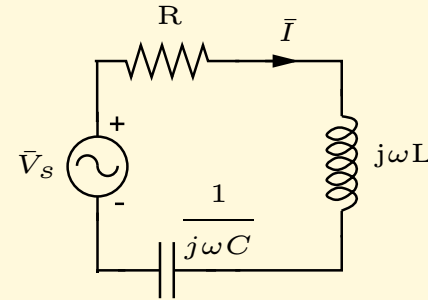


$$v_s(t) = 100 \sin(2\pi 50t) \text{ V}$$

$$\rightarrow \bar{V}_s = 70.71 \angle 0^\circ \text{ V}$$

$$i(t) = 5.27 \sin(2\pi 50t + 58.2^\circ) \text{ A}$$

$$\rightarrow \bar{I} = 3.727 \angle 58.2^\circ \text{ A}$$

Phasor Diagram

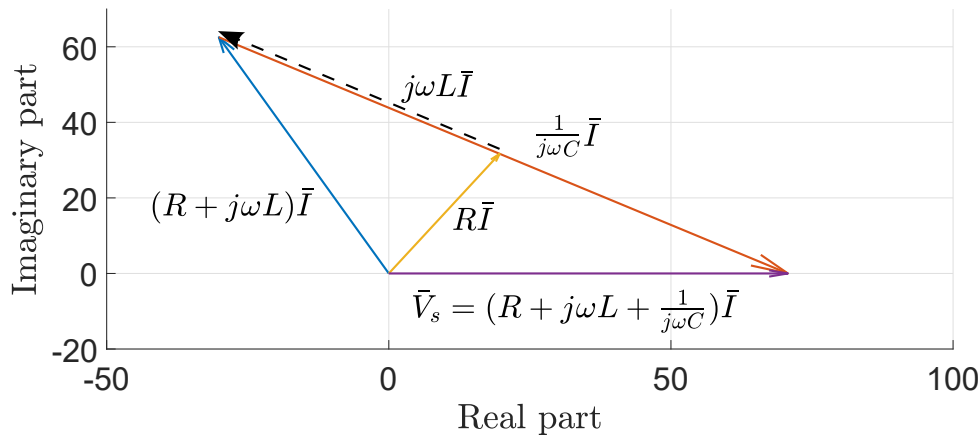

5. What is Reactive Power?

Consider a single phase system with

$$v_s(t) = V_m \sin(\omega t) \quad \text{and} \quad i(t) = I_m \sin(\omega t - \phi):$$

Then the **instantaneous power** is given as:

$$p(t) = v_s(t) \times i(t)$$


$$p(t) = V_m I_m \sin(\omega t) \sin(\omega t - \phi)$$

$$= \frac{1}{2} V_m I_m [\cos(\phi)(1 - \cos(2\omega t)) - \sin(\phi) \sin(2\omega t)]$$


$$\text{Real Power (or Average P)} = \frac{1}{2} V_m I_m \cos(\phi)$$

$$\text{Reactive Power (Q)} = \frac{1}{2} V_m I_m \sin(\phi)$$

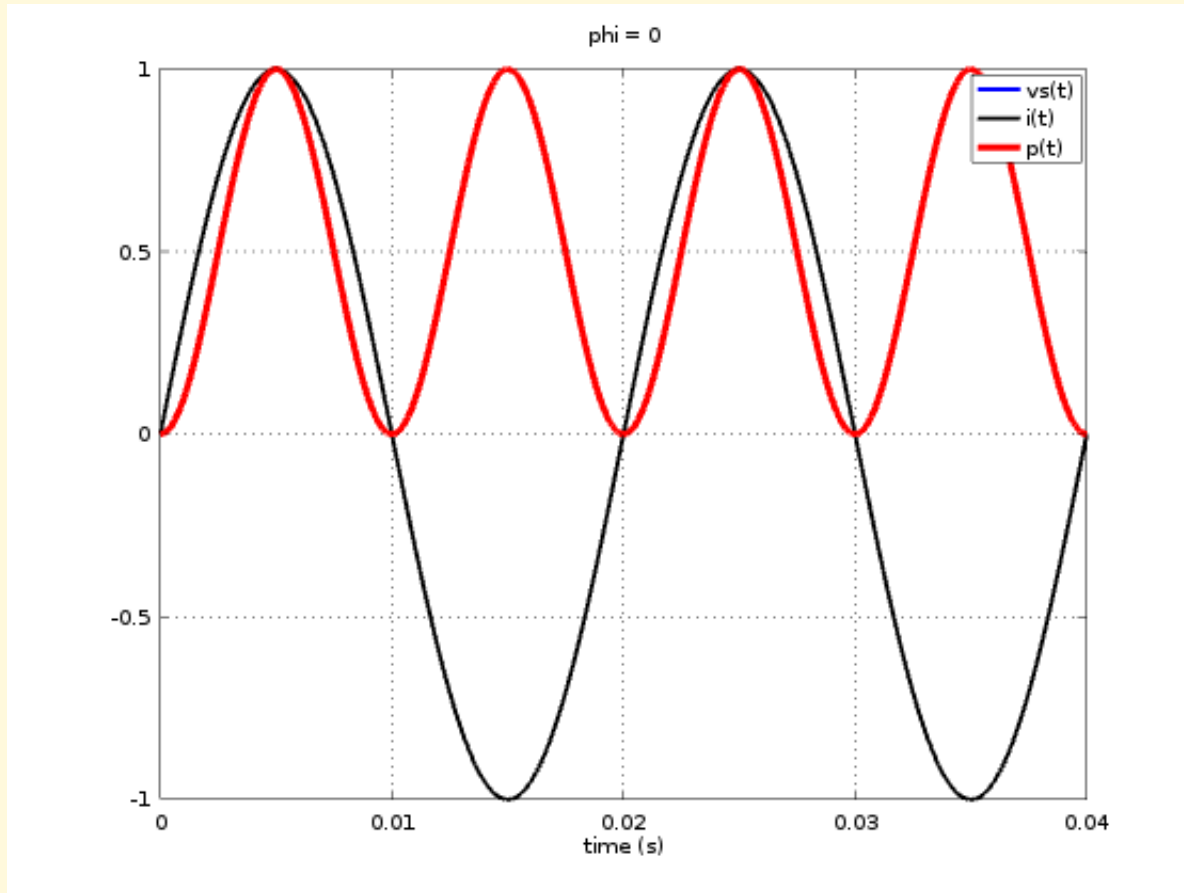
Instantaneous power for $\phi = 0^\circ$:



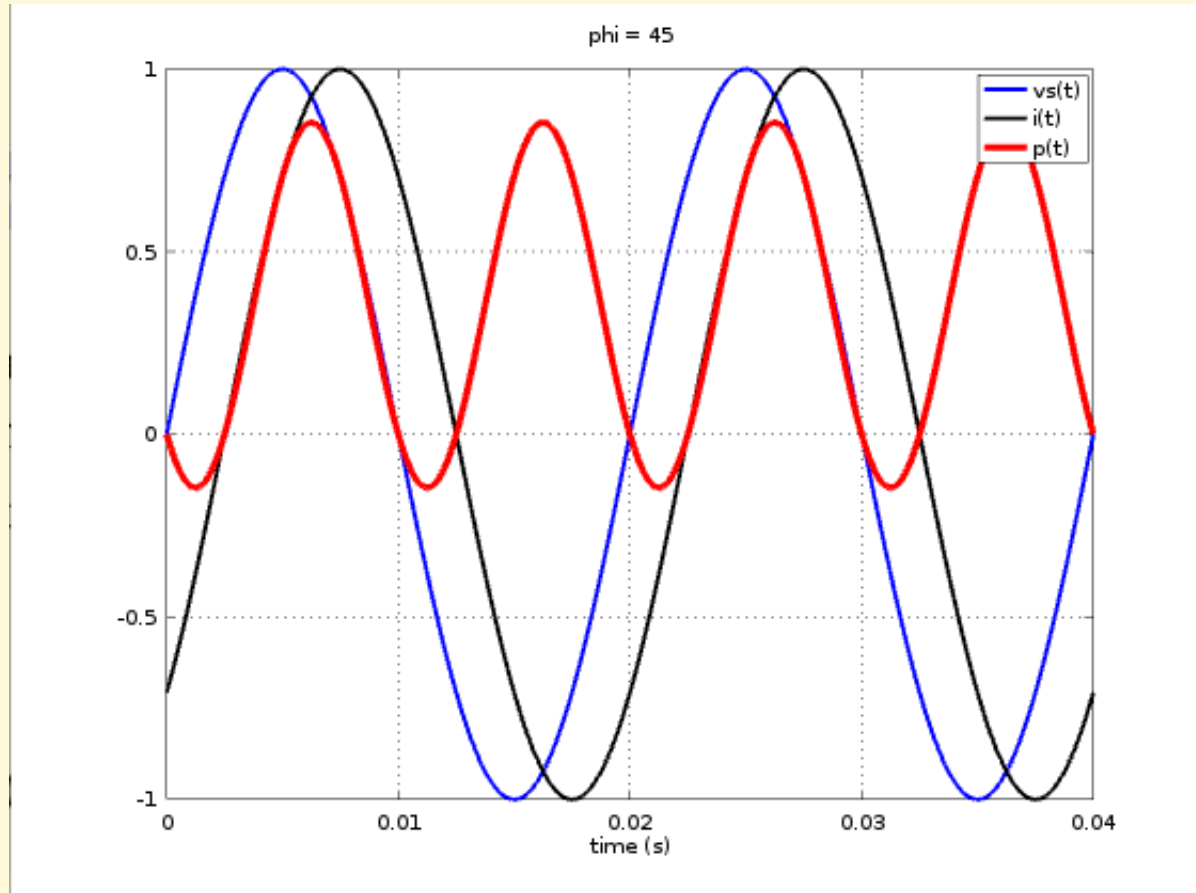
Instantaneous power for $\phi = 45^\circ$:



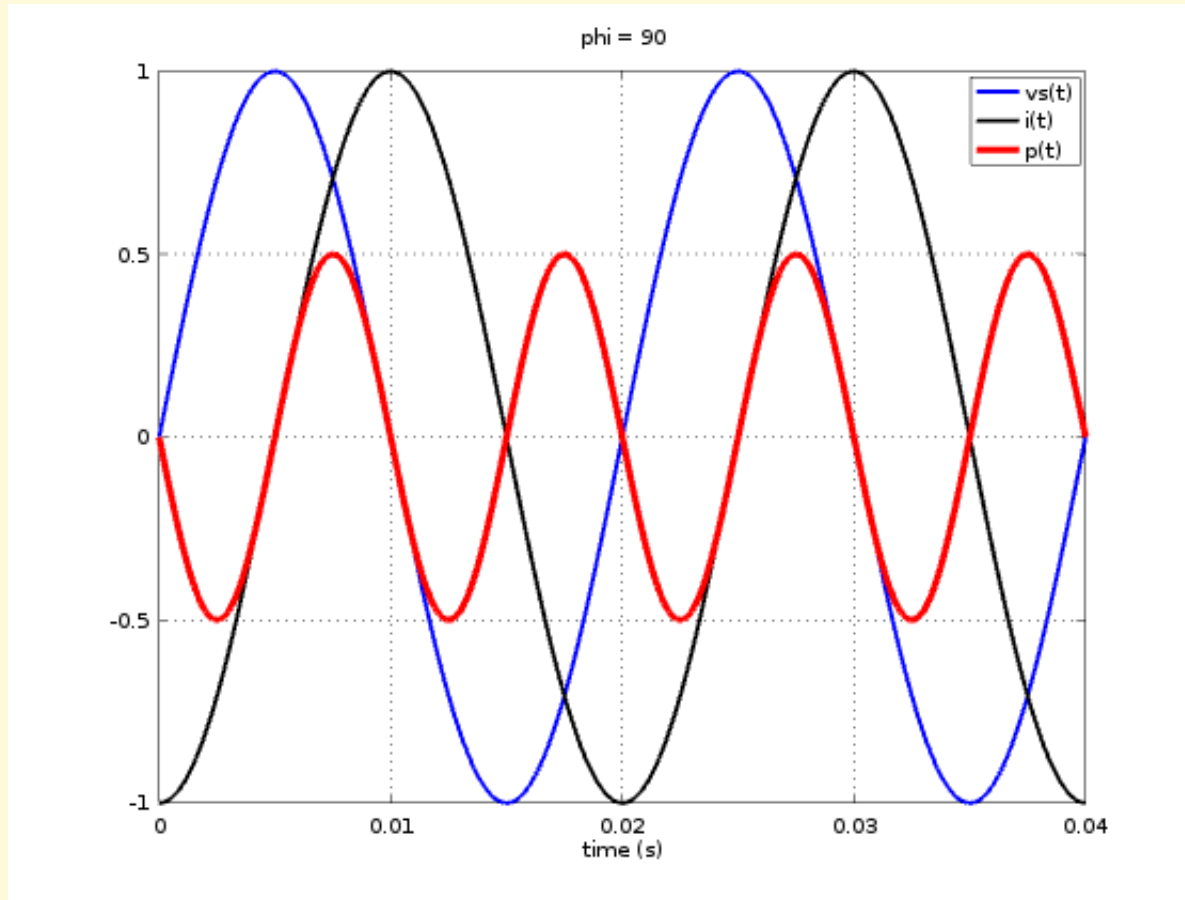
Instantaneous power for $\phi = 90^\circ$:



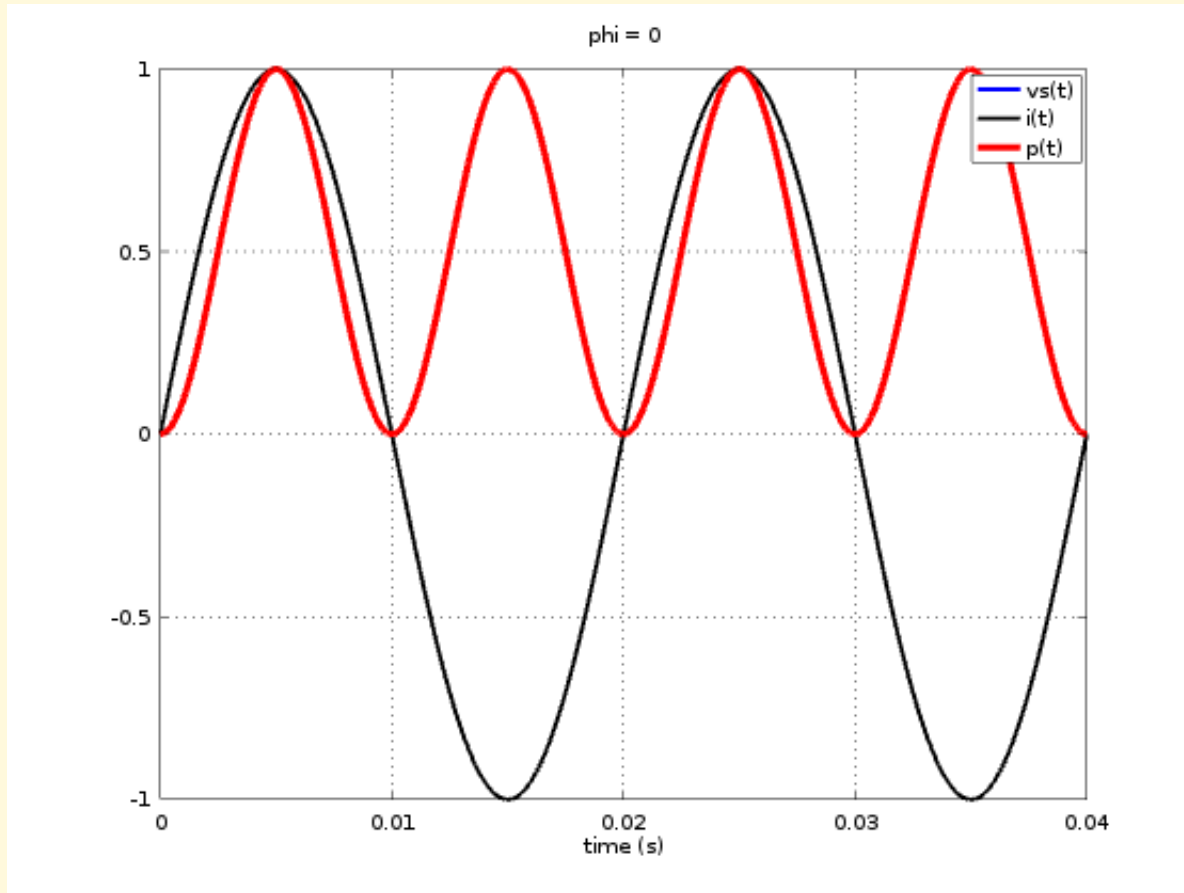
Instantaneous power for $\phi = 0^\circ$:



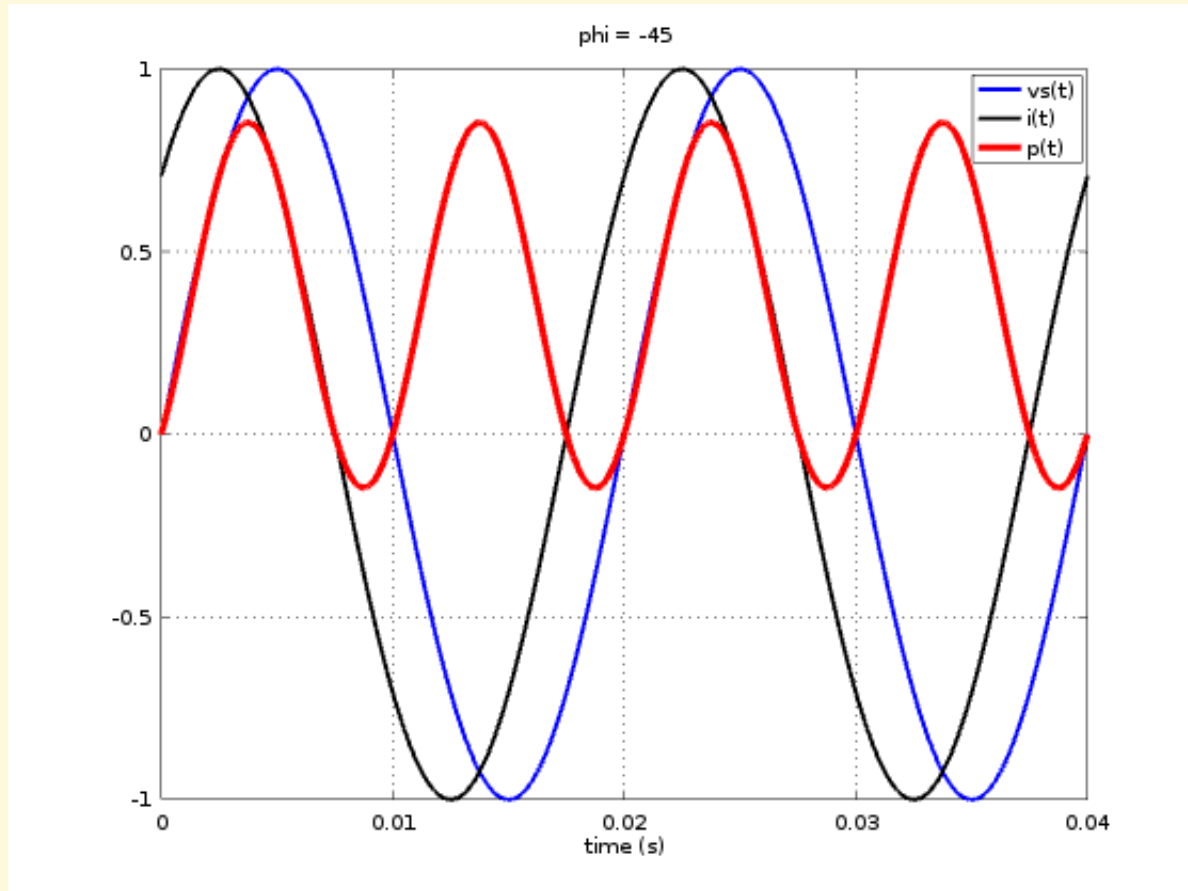Instantaneous power for $\phi = -45^\circ$:



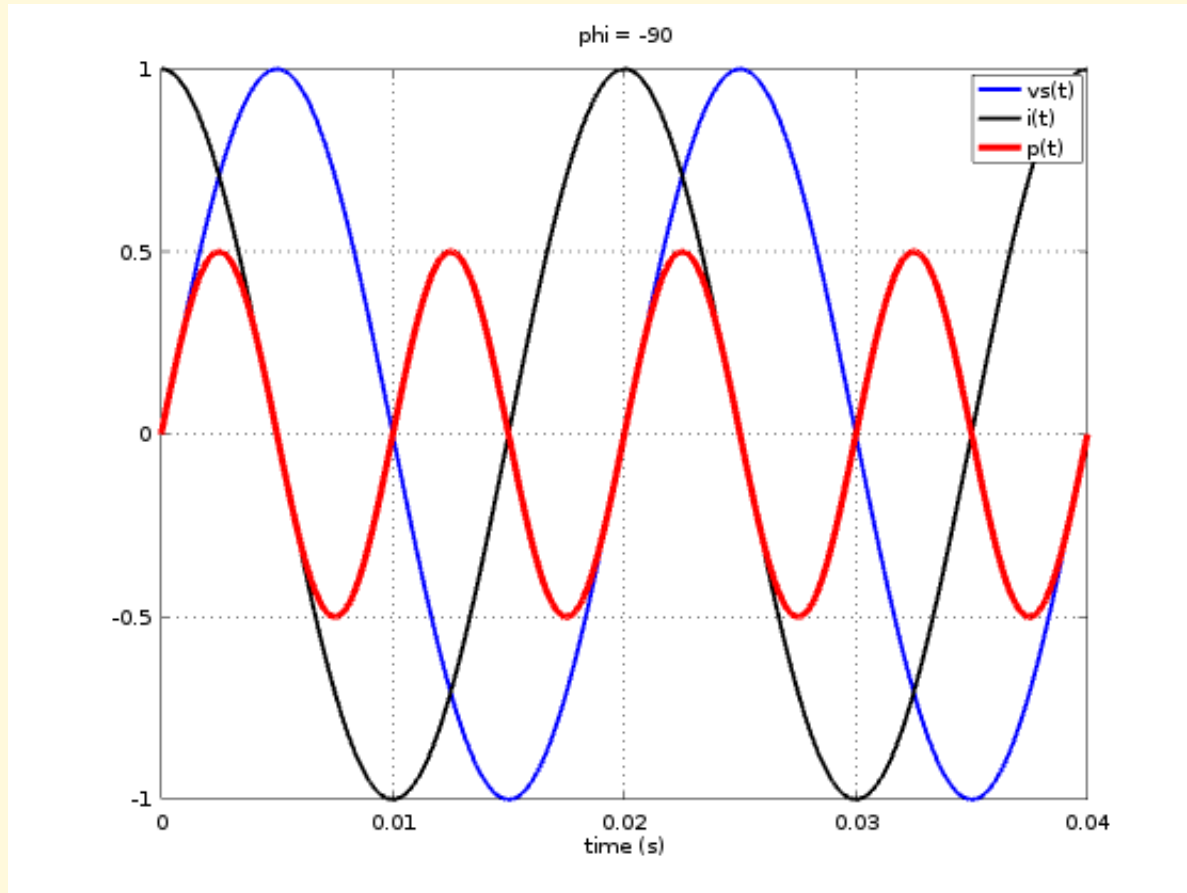Instantaneous power for $\phi = -90^\circ$:



6. Significance of Reactive Power

- Single phase instantaneous power is always **pulsating** at twice the supply frequency.
- If $\phi = 0^\circ$, then instantaneous power is always **positive** (resistor) and $\mathbf{Q} = \mathbf{0}$.
- If $\phi = \pm 90^\circ$, then only a **zero average pulsating** component is present (capacitor, inductor) and $\mathbf{P} = \mathbf{0}$.
- Also note that:

$$\tan(\phi) = \frac{Q}{P}, \quad \frac{1}{2}V_m I_m = S = \sqrt{P^2 + Q^2}$$

Significance of Reactive Power

- Phasor analysis can be used: Sum of S absorbed by all branches connected to a node=0

$$S = P + jQ = \bar{V}_s \times \bar{I}^*.$$


- $S > P$ when 'reactive elements are present. Implies that more current is drawn for same amount of P . Results in **more losses, more voltage drops and bigger equipment** for same P rating.
- An inductor “absorbs” **positive reactive power**;
a capacitor **absorbs negative reactive power** and vice - versa for supply.

7. Production & Absorption of Reactive Power

- **Synchronous Generators** : Can **generate** or **absorb** reactive power.
- **Overhead Lines** : **Absorb** or **supply** reactive power.
- **Cables** : **Generate** reactive power.
- **Transformers** : Always **absorb** reactive power.
- **Loads** : Normally **absorb** reactive power.
- **Compensating Devices** : **absorb** or **supply** reactive power.

Quick revision:

Time-domain

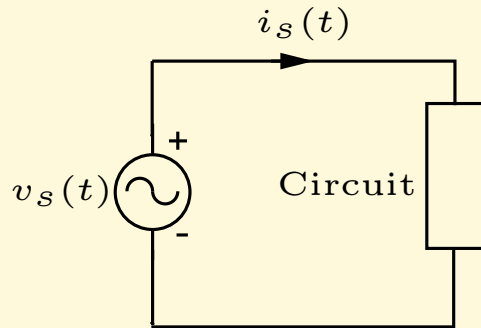


$$v_s(t) = V_m \sin(\omega t + \alpha) \text{ V}$$

$$i_s(t) = \frac{V_m}{|Z_{eq}|} \sin(\omega t + \alpha - \angle Z_{eq})$$

$$= I_m \sin(\omega t + \alpha - \phi) \text{ A.}$$

Phasor domain

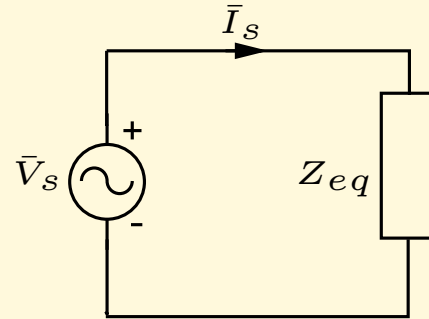

$$\bar{V}_s = \frac{V_m}{\sqrt{2}} \angle \alpha^\circ = V_{rms} \angle \alpha^\circ \text{ V}$$

$$\begin{aligned} \bar{I}_s &= \frac{V_m}{\sqrt{2}} \angle \alpha^\circ \cdot \frac{1}{Z_{eq}} = \frac{V_{rms} \angle \alpha^\circ}{Z_{eq}} \\ &= \frac{I_m}{\sqrt{2}} \angle (\alpha - \phi)^\circ = I_{rms} \angle (\alpha - \phi)^\circ \text{ A.} \end{aligned}$$

Z_{eq} is the equivalent impedance seen by the source.

Quick revision:

Time-domain

Instantaneous Power

$$p(t) = v_s(t) \times i_s(t)$$

$$p(t) = \frac{1}{2} V_m I_m [\cos \phi (1 - \cos(2\omega t)) - \sin \phi \sin(2\omega t)]$$

Average Power:

$$P = \frac{1}{T} \int_0^T p(\tau) d\tau = \frac{V_m I_m}{2} \cos \phi$$

$$P = V_{rms} I_{rms} \cos \phi$$

$$\text{Note: } T = \frac{2\pi}{\omega}$$

Phasor domain

Average Power is also found to be:

$$\begin{aligned} P &= \text{Real}\{\bar{V}_s \bar{I}_s^*\} \\ &= \text{Real}\{V_{rms} \angle \alpha (I_{rms} \angle (\alpha - \phi))^*\} \\ &= \text{Real}\{V_{rms} \angle \alpha (I_{rms} \angle (\phi - \alpha))\} \\ &= V_{rms} I_{rms} \cos \phi \end{aligned}$$

Note: P is Real or active power.

Q is defined as:

$$Q = \text{Imag}\{\bar{V}_s \bar{I}_s^*\} = V_{rms} I_{rms} \sin \phi.$$

Define:

$$\bar{S} = P + j Q = \bar{V}_s \times \bar{I}_s^*$$

$$S = \sqrt{P^2 + Q^2} = V_{rms} I_{rms}$$

$$\tan \phi = \frac{Q}{P}$$

where,

S : apparent power in **VA** (volt ampere)


P : **real / active / average power** in **W** (watt)

Q : **reactive power** in **VAR** (volt ampere reactive)

$$\cos \phi = \frac{P}{S} = \text{power factor.}$$

Convention for power calculations

Time-domain

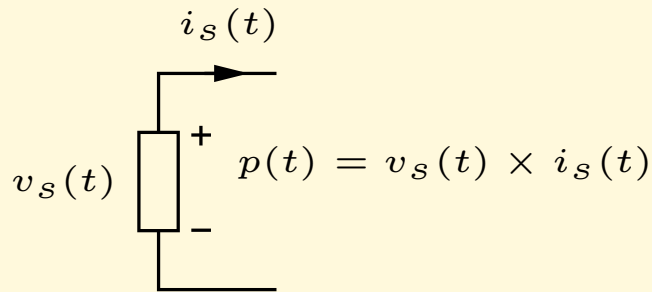


If at any time instant:

$p(t) > 0$: instantaneous power is **delivered**.

$p(t) < 0$: instantaneous power is **absorbed**.

Note: the voltage polarity and the sense of current flow.

Phasor domain

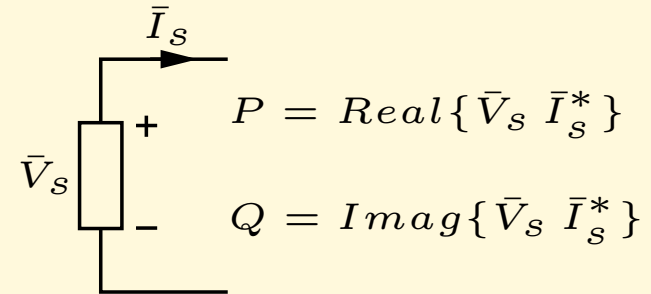

In steady state:

$P > 0$: average power is **delivered**.


$P < 0$: average power is **absorbed**.

$Q > 0$: reactive power is **delivered**.

$Q < 0$: reactive power is **absorbed**.

Convention for power calculations

Time-domain

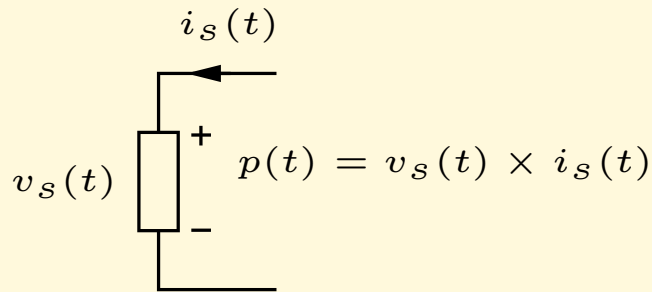


If at any time instant:

$p(t) > 0$: instantaneous power is **absorbed**.

$p(t) < 0$: instantaneous power is **delivered**.

Note: the voltage polarity and the sense of current flow.

Phasor domain

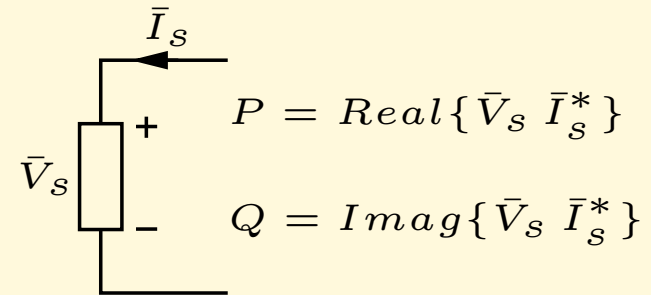

In steady state:


$P > 0$: average power is **absorbed**.

$P < 0$: average power is **delivered**.

$Q > 0$: reactive power is **absorbed**.

$Q < 0$: reactive power is **delivered**.

Power balancing in AC circuits

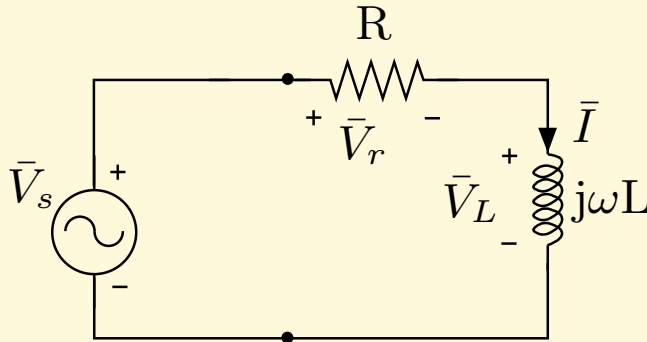

$$R = 10 \, \Omega, \quad L = 30 \, \text{mH}$$
$$\bar{V}_s = 100 \angle 30^\circ \, \text{V (rms value)}$$
$$\omega = 2\pi 50 = 314.16 \, \text{rad/s}$$

Circuit-1:

Solution:

$$\bar{I} = \frac{\bar{V}_s}{R + j\omega L} = 7.277 \angle -13.3^\circ \, \text{A}.$$

$$\bar{V}_r = R \times \bar{I} = 72.77 \angle -13.3^\circ \, \text{V} \quad \text{and} \quad \bar{V}_L = j\omega L \times \bar{I} = 68.584 \angle 76.7^\circ \, \text{V}$$


Apparent power **supplied** by source: $S_s = \bar{V}_s \bar{I}^* = (529.55 + j499.08) \, \text{VA}$

Apparent power **absorbed** by the resistor: $S_R = \bar{V}_r \bar{I}^* = (529.55 + j0) \, \text{VA}$

Apparent power **absorbed** by the inductor: $S_L = \bar{V}_L \bar{I}^* = (0 + j499.085) \, \text{VA}$

Supplied apparent power = Absorbed apparent power in the circuit.

Circuit-2:

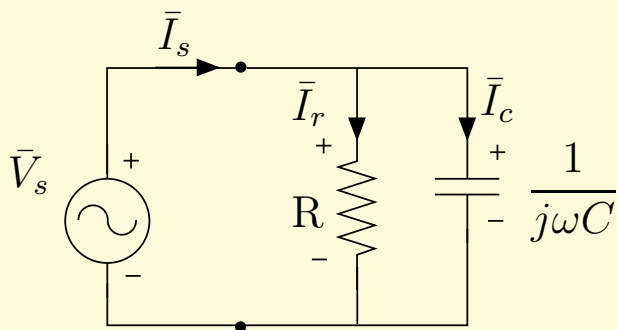

$$R = 10 \, \Omega, \quad C = 0.5 \, \text{mF}$$

$$\bar{V}_s = 100\angle 30^\circ \, \text{V (rms value)}$$

$$\omega = 2\pi 50 = 314.16 \, \text{rad/s}$$

Solution:

$$\bar{I}_r = \frac{\bar{V}_s}{R} = 10\angle 30^\circ \, \text{A} \quad \text{and} \quad \bar{I}_c = \frac{\bar{V}_s}{\left(\frac{1}{j\omega C}\right)} = 15.708\angle 120^\circ \, \text{A}$$

$$\bar{I}_s = \bar{I}_r + \bar{I}_c = 18.621\angle 87.52^\circ \, \text{A}.$$

Apparent power **supplied** by source: $S_s = \bar{V}_s \times \bar{I}_s^* = (999.96 - j1570.83) \, \text{VA}$


Apparent power **absorbed** by the resistor: $S_R = \bar{V}_s \times \bar{I}_r^* = (1000 + j0) \, \text{VA}$

Apparent power **absorbed** by the capacitor: $S_c = \bar{V}_s \times \bar{I}_c^* = (0 - j1570.8) \, \text{VA}$

Supplied apparent power = Absorbed apparent power in the circuit.

(Note: the numerical precision of calculations.)

Circuit-2:

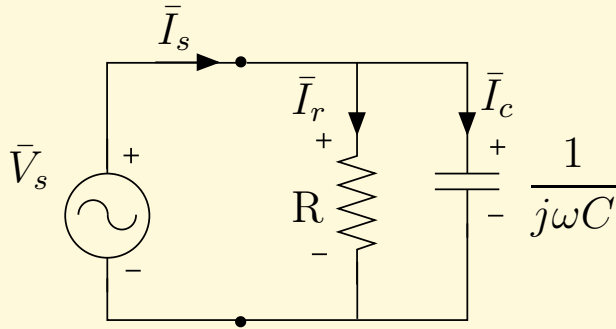

$$R = 10 \, \Omega, \quad C = 0.5 \, \text{mF}$$


$$\bar{V}_s = 100 \angle 30^\circ \, \text{V (rms value)}$$

$$\omega = 2\pi 50 = 314.16 \, \text{rad/s}$$


$$\bar{I}_r = 10 \angle 30^\circ \, \text{A}, \quad \bar{I}_c = 15.708 \angle 120^\circ \, \text{A}$$

$$\bar{I}_s = 18.621 \angle 87.52^\circ \, \text{A}.$$

Phasor Diagram

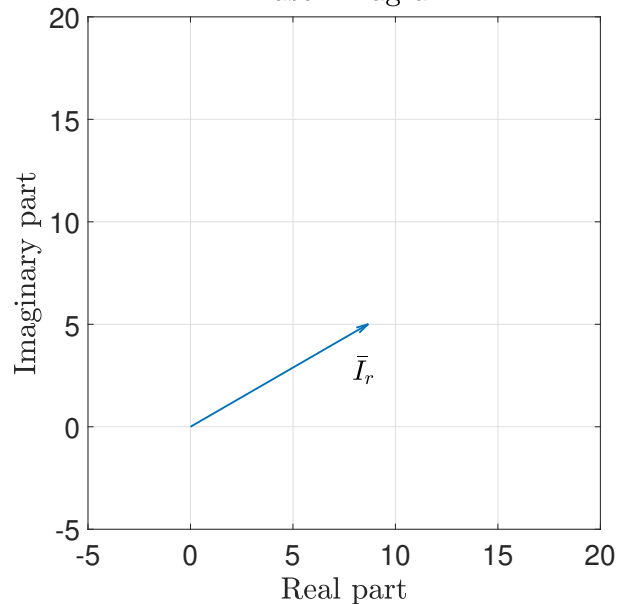

Circuit-2:

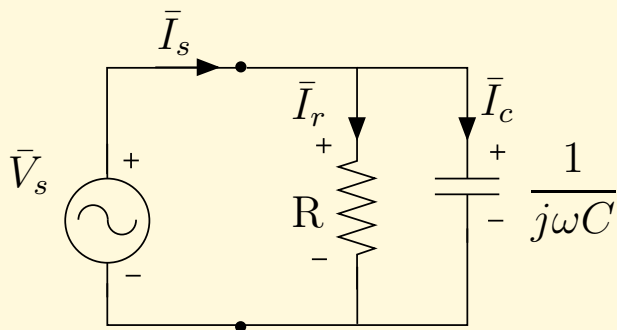


$$R = 10 \, \Omega, \quad C = 0.5 \, \text{mF}$$

$$\bar{V}_s = 100 \angle 30^\circ \, \text{V (rms value)}$$


$$\omega = 2\pi 50 = 314.16 \, \text{rad/s}$$

$$\bar{I}_r = 10 \angle 30^\circ \, \text{A}, \quad \bar{I}_c = 15.708 \angle 120^\circ \, \text{A}$$
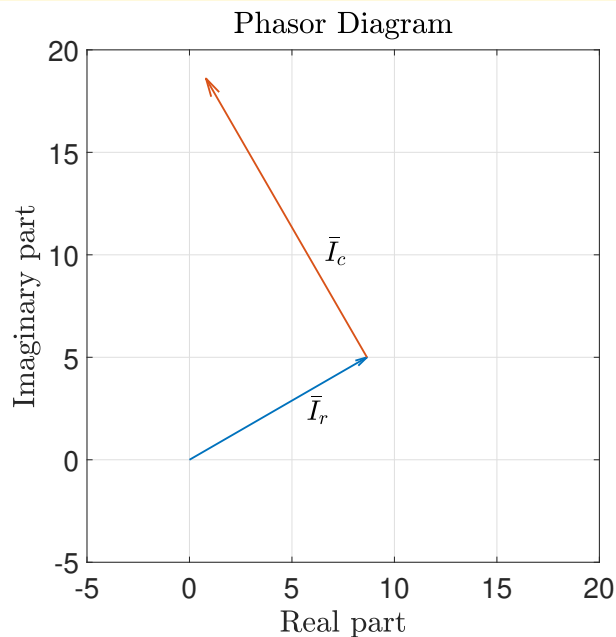
$$\bar{I}_s = 18.621 \angle 87.52^\circ \, \text{A}.$$



Circuit-2:

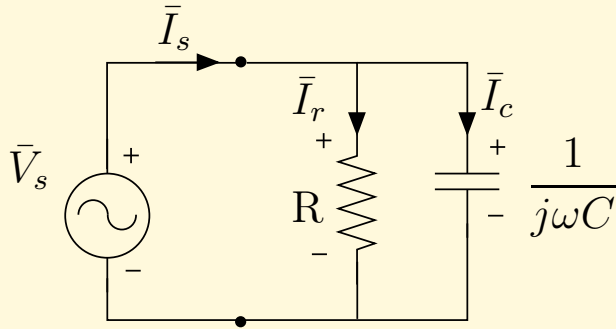

$$R = 10 \, \Omega, \quad C = 0.5 \, \text{mF}$$

$$\bar{V}_s = 100 \angle 30^\circ \, \text{V (rms value)}$$

$$\omega = 2\pi 50 = 314.16 \, \text{rad/s}$$

$$\bar{I}_r = 10 \angle 30^\circ \, \text{A}, \quad \bar{I}_c = 15.708 \angle 120^\circ \, \text{A}$$

$$\bar{I}_s = 18.621 \angle 87.52^\circ \, \text{A}.$$

